

LECTURE NOTES
ON
MICROPROCESSOR
&
MICRO CONTROLLER
SEMESTER-4TH

Prepared By: Abhaya Ghosh

Unit - 4

Microprocessor based system development aids

Interfacing:-

→ It is a mp used to connect it with various peripheral to perform various operation to obtain a desired O/P.

There are 2 types of interfacing.

(i) Memory interfacing

(ii) I/O interfacing


Memory Interfacing

→ It is used when the mp need to access the memory frequently for reading & writing data store in memory.

→ It is also used when writing & reading to a specific register of a memory chip.

I/O mapped I/O :-

 - Different address space require.
- Separate read & write control signal.
- I/O control signal is also used to control read & write operation.
- Processor provide separate address range for memory or I/O.
- Ex:- IN, OUT



Memory Interfacing:-

- Microprocessor 8085 can access 64KB memory since address bus is 16 bit. But it is not always necessary to use full 64KB address space. The total memory size depends upon the application.
- Generally EPROM is used as program memory & RAM is used as a data memory. When both EPROM & RAM are used the total address space 64KB that share by them.
- The capacity of data memory & program memory depends on the application.
- It is n't always necessary to select

One EPROM or one RAM, we can have multiple EPROM & multiple RAM as per the requirement of the application.

→ We can place EPROM or RAM anywhere in 64KB bus address space but the program memory should be located from address 000H & rest address of 8085 MP.

→ It is n't always necessary to locate EPROM & RAM in consecutive memory location.

• The memory interfacing required:-

→ Select the chip

→ Identify the registers

→ Enable the appropriate buffers.


→ MP system include memory device & I/O device. It is imp to note that mp can communicate with one device at a time, since the data, address & control buses are common for all devices.

→ In order to communicate with the memory or I/O device it is necessary to decode the address from the mp due each device can be access independently.

Address Decoding Technique

- There are 2 types of address decoding technique. (i) Absolute / Full decoding (ii) Partial / Linear decoding
- With absolute decoding, we use all address line ($A_0 - A_7$) for decoding of I/O devices.
- With partial decoding, few address line are not used for decoding I/O device.
- With absolute decoding we have six address for decoding I/O.
- With partial decoding multiple addresses may be decode.
- Absolute & Partial decoding may happen in case of memory interface.

8255 Programmable Peripheral Interface

 


- 8255 is a peripheral programmable interface.
- It was developed & manufacture by Intel corporation in 1970.
- It is also called as 8255A.
- 8255 PPI is the interface betⁿ mp & I/O device to connect peripheral device.

Feature of 8255 PPI :-

- 8255 is design to work with various mp like :- 8085, 8086.
- It is design to increase capacity of I/O interface.
- It is used 3 ports i.e, Port A, Port B, Port C.

Pin diagram :-

 

Continuing of A₀, A₁ Select

A ₀	A ₁	Select
0	0	Port A
0	1	Port B
1	0	Port C
1	1	Control register

- The selection of I/O port & control word register is done by using A₀, A₁.

8255 is a 40 IC pin package & these pins can be divided into 4 categories.

(i) Port

(ii) Data bus

(iii) Power Supply

(iv) Control Signal

Port:-

→ It is generally a specific place for being physically connected to the other devices using a socket & plug in computer, generally two ports are used:

(i) Serial Port

(ii) Parallel Port

Serial Port:-

Transmit 16 bit data at a time in sequence order.

Ex:- Scanner

Parallel Port:-

→ Transmit more than 16 bit data at a time parallelly.

Ex:- Printer

→ 8255 has 4 Port :- (i) Port A

(ii) Port B

(iii) Port C

(iv) Control Signal

→ $PA_0 - PA_7$ = Port A (8 bit)

→ $PB_0 - PB_7$ = Port B (8 bit)

→ $PC_0 - PC_3$ = Port C (lower) - 4 bit

→ $PC_4 - PC_7$ = Port C (upper) - 4 bit

Data bus

- It is a 8bit bus i.e, $D_0 - D_7$ & it is also called bidirectional & pin occurring 27 to 34 in the 8255 diagram.

Power Supply:-

- 8255 PPI uses +5V power supply as V_{CC} & 26 no. 06 pin use for the V_{CC} & 7 no. pin as ground (GND) pin.

Control Signal:-

$\overline{CS}$ (Chip select)

- A low i/p signal enable, the communication betⁿ 8255 & CPU.

$\overline{WR}$ (Write)

It is an active low signal. It performs write operation when the signal goes low, the mp write into a selected i/p or o/p port & a control word register.

$\overline{RD}$ (Read)

It is an active low signal. It performs read operation when the signal goes low, the mp read into a selected i/p or o/p port & a control word register.

RESET

It is an active high signal. It clear the control word register & save all port in the i/p port.

A_1, A_0

These are normally connected to the lower bit of address bus i.e, $A_0 - A_1$ & occupying the pin 8 & 9.

Operating mode of 8255:-

There are 2 different operating mode for 8255 PPI.

- (i) Bit set or Reset mode
- (ii) I/O mode

BSR mode:-

It is mainly used to define handshake signal.

I/O mode:-

It is used for input or output data transfer.

Control word Register

- 8255 may be operated in one of the 2 mode (BSR or I/O mode) by initializing D₇ bit.
- If D₇ bit = 1 then it is operating in I/O mode.
- If D₇ = 0 then it is operating in BSR mode.

Input or Output Mode

This mode is divided into 3 types.

(i) mode 0

(ii) mode 1

(iii) mode 2

Mode 0

- It is a simple I/O mode.
- In this mode Port A, Port B, Port C are used as simple 8bit I/O port.
- This port couldn't need/require handshaking signal.
- There is no need of BSR mode, that's why we are using I/O mode in this mode.


Mode 1

- It is also known as strobed I/O mode.
- When Group A & Group B are programmed to mode 1 then two ports operated in strobed in mode, to this burst of all control word registers to BSR mode to derive the strobe signal as handshaking.
- After that the control word register is program to I/O mode.

Mode 2

- It is also known as bi-direction handshaking I/O.
- In this mode port A is used as bi-direction mode & port B is either on mode 0 or mode 1.

Block Diagram of 8255 PPI

 

BSR

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	X	X	X				

It is used to

Select pin of port C

It is set/reset

pin of port C

- D₇ bit is always 0 in BSR mode.
- BSR mode is always applicable to port C only (PC₀-PC₇).
- Each line of port C can be set or reset by loading in control word register.
- Bit D₆, D₅, D₄ are unspecified. Bit D₃, D₂, D₁ are used to select the pin of port C. D₀ bit is used to set or reset the pin of port C.

I/O Mode :-

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
1							

Mode selection
group A

Mode selection group B

- This mode is selected when D₇ bit is one.
- There are 3 I/O mode
 - (i) Mode 0 (Simple I/O)
 - (ii) Mode 1 (Strobed I/O)
 - (iii) Mode 2 (Strobed I/O bidirectional)
- D₀, D₁, D₃, D₄ are assign for port C lower, port B, port C upper & port A respectively.
- If D₀=D₄=0, the port C lower & port A is act as o/p port. If D₀=D₄=1, the port C lower & port A act as i/p port.

→ If $D_1 = D_3 = 0$, then port B & port C upper act as o/p port. If $D_1 = D_3 = 1$, then port B & port C upper act as i/p port.

→ D_2 is used for the mode selection of group B (port B & port C lower).

→ When $D_2 = 0$, mode 0 is selected & when $D_2 = 1$, mode 1 is selected.

→ D_5 & D_6 are used for the mode selection of group A (Port A, Port C upper).

→ Mode selected n bit D_2, D_5, D_6 are all 0 for mode 0 operation.

Control word

	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	Bit no
Control word Register				Port A	Port C Upper	Mode for Port B	Port B	Port C lower	

→ Control word is used for the programming port of 8255. The control word is written into the control word register.

→ No read operation of the control word register is allowed. If a particular port is to be made an i/p port the corresponding bit for the port is said to 1.

→ If a particular port is made an o/p port the corresponding bit for the port is set to 0.

Control Group

→ The 24 line of i/p port are divided into 2 groups i.e., group A & group B.

→ The group A contains port A & port C upper.

→ The group B contains port B & port C lower.

Bit no (D₀) [It is for port C lower]

→ To make port C lower an i/p port, the bit set to 1.

→ To make port C lower an o/p port, the bit set to 0.

Bit no (D₁) [It is for port B]

→ To make port B an i/p port the bit is set to 1.

→ To make port B an o/p port the bit is set to 0.

Bit no (D₂) [It is for selection of the mode for the port B]

It is for the selection of the mode for the port B. If the port B operated as mode 0 the bit is set to 0 & for mode 1 operation of the port B, it is set to 1.

Bit no (D₃) [It is for port C upper]

→ To make port C upper an i/p port, the bit is set to 1.

→ To make port C upper an o/p port, the bit is set to 0.

Bit no (D₄) [It is for port A]

→ To make port A an i/p port; It is set to 1.

→ To make port A an o/p port, It is set to 0.


Bit no. D5, D6

→ This bit is used to define the operating mode of port A.

Mode of Port A	Bit no 6	Bit no 5
MODE 0	0	0
MODE 1	0	1
MODE 2	1	0/1

* Absolute Decoding / Full Decoding

 
In this technique, all the higher address lines are decoded to select the memory chip & the memory chip is selected only for the specified logic levels on these higher order address lines, no other logic levels can select the chip. Below figure shows the memory interfacing in 8085 with absolute decoding. This is normally used in large memory systems.



Linear Decoding

In small systems, hardware for the decoding logic can be eliminated by using individual high-order address lines to select memory chips. This is referred to as linear decoding. Below fig. shows the addressing of RAM with linear decoding technique. This is also called partial decoding. It reduces the cost of decoding circuit, but it has a drawback of multiple addresses (shadow address).

A15 address line is directly connected to the chip select signal of EPROM & after inversion it is connected to the chip select signal of the RAM. Therefore, when the status of A15 line is 'zero', EPROM gets selected & when the status of A15 line is 'one' RAM gets selected. The status of the other address lines are not considered, since those address lines are not used for generation of chip select signals.

 


* Memory Interfacing in 8085


- Memory is an integral part of a μp system.
- Memory interfacing in 8085 is used to access memory quite frequently to read instruction codes & data stored in the memory.
- These read/write operations are monitored by control signals.
- The μp activates these signals when it wants to read from & write into memory.

Memory structure & its requirement

 - Read/write memories consist of an array of registers in which each register has a unique address.
- The size of the memory is $N \times M$ as shown in below figure where N is the number of registers & M is the word length, in number of bits.





LOGIC DIAGRAM FOR RAM

 

LOGIC DIAGRAM FOR EPROM

ADC & DAC with Interfacing:-

ADC (Analog to Digital Converter)

  

- It is an electronic IC which transforms analog signal (continuous) to digital signal (discrete).
- Analog signals are directly measurable quantities while digital signals only have two states that is 0 & 1.

Purpose of ADC

- Processor perform arithmetic operations on digital signals.
- Signals in digital form are less susceptible to effect of noise.
- ADC provides link betⁿ analog signal & digital signal.
- Following are the types of analog to digital converter (ADC):- Counter type, Successive approximation, Flash ADC, Sigma & delta.

Application of ADC :-


Digital voltmeter - It measures voltage in analog & convert to digital form using ADC for digital representation form.

Mobile Phone - Analog voice is converted to digital form for further processing (speech operation encoding etc.). Before it is converted, back to analog form for transmission.

Scanner - When we take photo or scan document the scanner uses ADC internally to convert analog information provided by picture / document into digital information.


Voice recorder - It uses ADC to convert analog voice information to digital information.

DAC (Digital to analog converter)

 

Digital signal

DAC

 

Analog signal

- To convert digital values to analog values.
- It performs inverse operation of ADC.
- There are 2 types of DAC
 - (i) Weighted Resistor
 - (ii) Resistive Divider

→ Following specifications are considered from the design, development as well as selection of DAC.

- Resolution
- Linearity
- Reference voltages
- Speed
- Settling time
- Errors

Application of DAC

→ Modem - Modem needs DAC to convert data to analog form. So that it can be carried over telephone wires.

→ Pointers

→ Digital audio

→ Digital motor control

→ Sound equipments

Data Transfer Schemes

In a μ p-based system or in a computer data transfer takes place betⁿ 2 devices such as μ p & memory, μ p & I/O devices, memory & I/O devices. Usually, memories are compatible with μ p because the same technology is employed in the manufacturing of both memories & μ ps. Hence, there is less problem associated with the interfacing of memory.

A μ p-based system or a computer may have several I/O devices of different speed. A slow I/O device can't transfer data when μ p issues instruction for the same because it takes some time to get ready. To solve the problem of speed mismatch betⁿ a μ p & I/O devices a no. of data transfer techniques have been developed.

The data transfer schemes are classified into the following two broad categories:

- i) Programmed data transfer schemes
- ii) DMA data transfer schemes.

Programmed Data transfer scheme:-

Programmed Data transfer schemes are controlled by the CPU. Data are transferred from an I/O device to the CPU or vice versa under the control of programs which reside in the memory.

These programs are executed by the CPU when an I/O device is ready to transfer data. The mp executes the program to transfer data. Programmed data transfer schemes are employed when small amount of data are to be transferred. The programmed data transfer schemes are classified into the following 3 categories.

- (i) Synchronous data transfer scheme
- ii) Asynchronous data transfer scheme
- iii) Interrupt driven data transfer scheme

Synchronous Data transfer scheme:-


- Synchronous means "at the same time".
- The device which receives data are synchronized with same clock.
- When the CPU, I/O devices match in speed, the synchronous data transfer is employed.
- The data transfer with I/O devices performed executing IN or OUT instruction for I/O mapped I/O devices or memory read/write instruction for memory.
- This technique is rarely used because I/O device compatible with mp in speed are usually not available.

Asynchronous Data Transfer :-

- Asynchronous means at regular intervals.
- In this method, data transfer is not based on predetermined timing pattern.
- This technique of data transfer is used when the speed of an I/O device doesn't match the speed of the mp.
- In this technique, the status of the I/O device i.e., whether the device is ready or not checked by the mp before the data transfer.

Purpose of Asynchronous Data transfer

 - Mp check the status signal before the data transfer.
- Then mp indicates the I/O device to get ready.
- When I/O device get ready the mp sends instructions to transfer the data.



- A Keyboard interfaced to a mp is an example of this type of data transfer scheme.


Asynchronous Data transfer scheme of an A/D converter

- Asynchronous data transfer is used for slow I/O device.
- An A/D converter has been transferred to the mp to transfer data in asynchronous mode.

Process:


- The mp sends a start or conversion signal S/C to the ADC.

 - The HV is so slow therefore it takes more time to convert analog signal to digital signal.
- When conversion is over ADC makes end of conversion signal. It means E/C signal is high.
- When E/C signal becomes high the mp issues instruction for data transfer.






Interrupt Driven Data transfer:

- In this scheme the mp initiates an I/O device to get ready & then it executes its main program instead of remaining in a program loop to check the status of the I/O device.
- It just interrupts the normal processing sequence of the mp.
- On receiving an interrupt the mp completes the current instruction at hand & then attends the I/O device.
- It saves the content of the Program Counter on stack then takes a subroutine called ISS.
- It executes ISS to transfer data from or to the I/O device.
- Different ISS are to be provided for different I/O device.
- After completing the data transfer the mp returns back to the main program.

 

Interfacing Seven Segment Displays

- Interfacing the 8085 mp system with 7 segment display through the programmed I/O port 8255.
 - 7 segment displays is often used in the digital electronic equipment to display information regarding certain process.
 - I/O devices such as LEDs & Keyboards are essential components of the mp based or microcontroller based system.
 - 7 segment LEDs often used to display BCD no.s (0 to 9) & a few alphabets.
 - A group of 8 LEDs physically mounted in the shape of the no eight plus a decimal point.
 - Each LED is called a segment & labeled as 'a' through 'g'.
 - Commonly used o/p peripherals in embedded systems are LEDs, 7 segment LEDs & LCDs, the simplest is LED.
- Two ways of connecting LEDs to I/O ports
- i) LED cathode are grounded & logic 1 from the I/O port turns on the LEDs. The current is supplied by the I/O port called current sourcing.
 - ii) LED anodes are connected to the power supply & logic 0 from the I/O port turns on the LEDs. The current is received by the chip called current sinking.
- In a common anode 7 segment LED, all anodes are connected together to a power supply & the cathodes are connected to data lines.

   

1. The 7447 BCD-to-7-segment decoder IC is used to convert the BCD input to the seven-segment display.

 2. The 8255 PPI IC is used to interface the 7447 BCD-to-7-segment decoder IC with the microcontroller.

 3. The 8255 PPI IC is configured as an 8-bit parallel I/O device.

 4. The 8255 PPI IC is connected to the microcontroller via the data bus (D0-D7), address bus (A0-A1), and control bus (CS, WR, RD).

 5. The 7447 BCD-to-7-segment decoder IC is connected to the 8255 PPI IC via the BCD input (D0-D3) and the Vcc and ground pins.

 6. The 7447 BCD-to-7-segment decoder IC is connected to the seven-segment display via the output lines (a-g).

 7. The seven-segment display is connected to the 7447 BCD-to-7-segment decoder IC via the output lines (a-g).

 8. The seven-segment display is labeled 'Seven segment Display' and 'od/p'.

prepared by Abhaya Ghosh

4.10

* Interfacing Stepper Motor with 8085

→ Stepper Motor is an electromechanical device that rotates through fixed angular steps when digital inputs are applied. It is suitable for precise position, speed & direction control which are required in automation system.

→ The angle through which stepper motor rotates with a fixed angle for each digital data is called step angle.

→ Different stepper motor has different step angle. The more frequently used stepper motor has step angle of 0.9 degrees & 1.8 degrees.

→ Depending on the sequence applied to stepper motor, it can be classified in 2 categories:

(I) 4-Step Sequence / Full step Sequence

(II) 8-Step Sequence / Half step Sequence

Excitation Sequence for clockwise & anti-clockwise rotation of Stepper motor

Motion	Steps	A	B	C	D
Clockwise	1	1	0	0	0
	2	0	1	0	0
	3	0	0	1	0
	4	0	0	0	1
	5	1	0	0	0

Motion	Steps	A	B	C	D
Anti-clock Wise	1	1	0	0	0
	2	0	0	0	1
	3	0	0	1	0
	4	0	1	0	0
	5	1	0	0	0

Program:-

~~H~~

LXI SP, 2800H

MVI A, 80H (Initialize 8255)

OUT 83H (CWR)

MVI B, 32H

Repeat: LXI H, 2100H

MVI C, 04H

Back: MOV A, M

OUT 80H (Port a)

CALL Delay

INX H


DCR C

JNZ Back

DCR B

JNZ Repeat




HLT

 

   4.9 Interfacing traffic light control with 8085

- Traffic lights alternate the right of way of road users by displaying lights of a standard color (red, yellow, green).
- The various control signals such as red, green, yellow, forward arrow, right arrow & left arrow are used in this scheme.


The traffic light control is implemented using the 8085 MP having 8255 on board.



Displays waiting Time

Each signal is controlled by a separate pin of I/O ports. The total no. of logic signals required for this arrangement is 24. The PPI device 8255 is used to interface these 24 logic signals with the lamps. The logic '0' & '1' represent the state of lamp. Logic '1'

 represent 1's ON & '0' represents OFF. All ports of 8255 are used as O/P ports.



Program

MVI A, 80H

OUT 83H (CR): in O/P mode

start: MVI A, 0AH

OUT 80H (CPA)

MVI A, 24H

OUT 81H (CPB)

MVI C, 28H

CALL Delay: call delay subroutine

MVI A, 12H

OUT PA

OUT PB

MVI C, 0AH

CALL Delay

JMP start

Delay Subroutine

Delay: LXI D, Count

BACK: DCXD

MOV A, D

ORA E (check whether Count=0)


JNZ BACK

DCR C


JNZ Delay

RET


(Return to main program)

 

 Generate Square waves on all lines of 8255



 - A square wave is a non-sinusoidal periodic waveform in which the amplitude alternates at a steady frequency between fixed min^m & max^m values, with the same duration at min^m & max^m.
- A square wave or pulse can easily be generated by mp. The mp sends high & then low signals to generate square wave or pulse. It can be generated using I/O port or SOD line or timer/counter.



The pin PBO of the Port B of 8255 is used for taking O/P. This is connected to a buffer 7407. The final O/P is taken from the buffer terminal. The control word used in the program is 98H to make Port B an O/P Port.

Program

LXI SP, 6000 (Initialize SP to use CALL)

MVI A, 98 (Control word or 82SS)

OUT 83 (Load the control word into 82SS)

LOOP: MVI A, 00 (Data for low pulse)

OUT 81 (Send PBo as low)

CALL Delay1

MVI A, 01

OUT 81 (Send PBo as high)

CALL Delay2

JMP LOOP

Subroutine

Delay1: MVI B, 10 (Count value)

LOOP1: DCR B

JNZ LOOP1

RET

Delay2: MVI C, 10

LOOP2: DCR C

JNZ LOOP2

RET