

Experiment - 1

AIM OF THE EXPERIMENT:

Introduction to digital electronics.

DEFINATION OF DIGITAL ELECTRONICS:

- i) Digital electronics is a branch of electronics that deals with two digits i.e. 0 & 1. Here, 0 means low logic or false and 1 means high logic or true.
- ii) Digital electronics involving study about the digital signal use and produce them.
- iii) Digital electronics operates to including different types of gates and that gates are binding with integral circuit.

REQUIREMENTS TO CONDUCT DIGITAL ELECTRONICS LAB:

- a) Digital electronics trainer kit.
- b) Power connection.
- c) Connector
- d) Gloves

ADVANTAGES OF DIGITAL ELECTRONICS:

- a) Digital systems are easier to design.
- b) Information storage is easy.
- c) Accuracy is very high.
- d) Digital circuits are less affected by noise.
- e) Easy to perform error detection and execution with digital signal.
- f) Integrated circuits are mostly used in the digital electronics, so that size of digital devices are small.

DISADVANTAGES OF DIGITAL ELECTRONICS:

- i) Heat will be more when digital circuits are working more time.
- ii) Digital circuits require a power supply.
- iii) Digital circuits consume more energy or power as compare to any circuits.
- iv) More complex circuits.
- v) When one IC will be damaged it must affect to others.

APPLICATION OF DIGITAL ELECTRONICS:

- i) Digital watch
- ii) Refrigerator
- iii) Speedometer
- iv) Traffic light
- v) Automatic glass door in offices and restaurant.
- vi) Rocket science.
- vii) ATM card
- viii) Computer & laptops.

CONCLUSION:

We concluded that the above experiment has been done by me successfully.

Experiment - 2

AIM OF THE EXPERIMENT:

To study about NOT gate.

APPARATUS REQUIRED:

- i) Digital electronics kit
- ii) Probes(connectors)
- iii) Power supply

TRUTH TABLE:

INPUT	OUTPUT
A	\overline{A}
0	1
1	0

CONCLUSION:

We concluded that the above experiment has been done by me successfully.

Experiment - 3

AIM OF THE EXPERIMENT:-

To study about OR gate

APPARATUS REQUIRED:-

- i. Digital trainer kit.
- ii. Probes (connector)
- iii. Power Supply.


TRUTH TABLE:-

Input		Output
A	B	$Q=A+B$
0	0	0
0	1	1
1	0	1
1	1	1


CONCLUSION:-

We concluded that the above experiment has been done successfully by us.

LOGIC GATE DIAGRAM:-

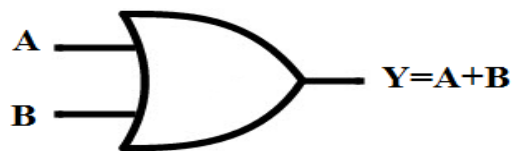

TIMING DIAGRAM:-

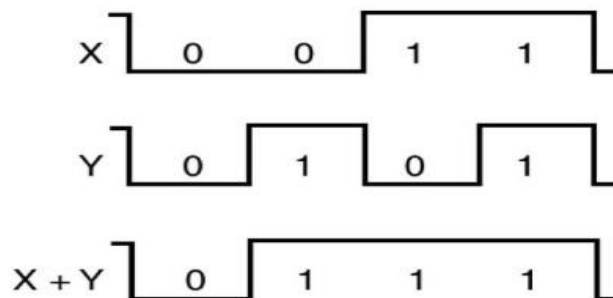

Experiment - 4

AIM OF THE EXPERIMENT:-

To study about AND gate.

APPARATUS REQUIRED:-

- i. Digital trainer kit
- ii. Probes(connectors)
- iii. Power supply


TRUTH TABLE:-

Input		Output
A	B	$Q=A.B$
0	0	0
0	1	0
1	0	0
1	1	1


CONCLUSION:-

We concluded that the above experiment has been done by us successfully.

AND GATE DIAGRAM:-

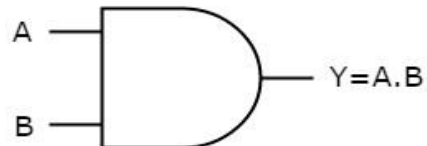

TIMING DIAGRAM:-

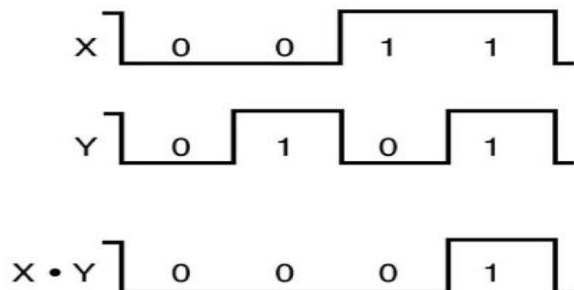

Experiment - 5

AIM OF THE EXPERIMENT:-

To study about NAND logic gate

APPARATUS REQUIRED:-

- i. Digital trainer kit
- ii. Probes(connection)
- iii. Power supply


TRUTH TABLE:-

INPUT		OUTPUT
A	B	$Q = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0


CONCLUSION:-

We concluded that the above experiment has been done by us successfully.

NAND gate diagram:-

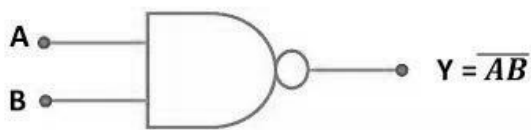

Timing diagram:-

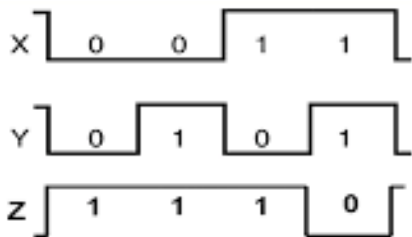

Experiment – 6

Aim of the experiment:-

To study about NOR logic gate

Apparatus Required:-

i) Digital trainer kit

ii) probes (connector)

iii) Power supply


Truth Table:-

INPUT		OUTPUT
A	B	$Q = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0


Conclusion:-

We conclude that the above experiment has been done by us successfully

Logic gate diagram:-

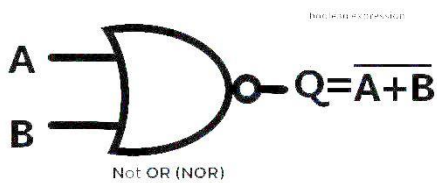

Timing diagram:-

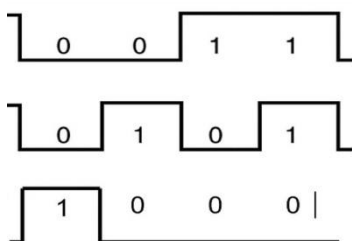

Experiment – 8

Aim of the Experiment-

To study about x-nor gate

Apparatus Required:-

- i) Digital trainer kit.
- ii) probes (connector).
- iii) power supply.

Truth Table:-

INPUT		OUTPUT
A	B	$Q=AB+\overline{AB}$
0	0	1
0	1	0
1	0	0
1	1	1

Conclusion:-

We concluded that the above experiment has been done by us successfully.

Experiment – 9a

AIM OF THE EXPERIMENT:-

To implement various gates by using universal properties of NAND gates, verify and truth table tabulate data.


APPARATAUS REQUIRED:-

- i) Digital electronic kit
- ii) Probes(connector)
- iii) Power supply

TRUTH TABLE:-


- i) NOT gate using NAND gate

Input	Output
A	Y
0	1
1	0

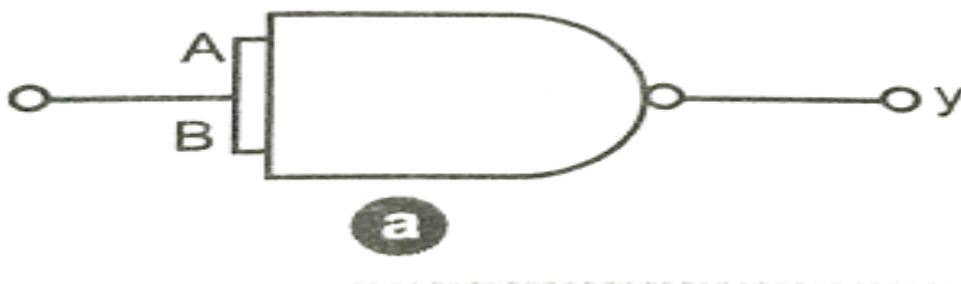


- ii) OR gate using NAND gate

Input		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

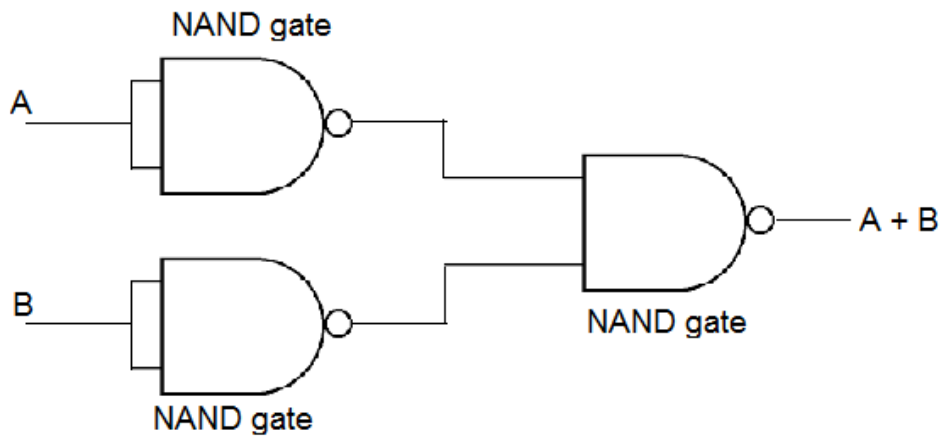


iii) AND gate using NAND gate

Input		Output
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

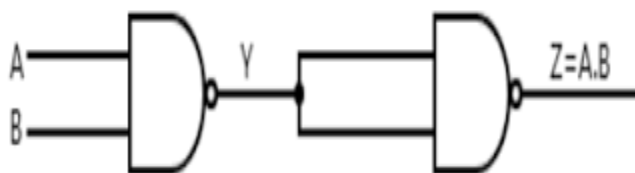


iv) X-OR gate using NAND gate

Input A	Input B	Output
0	0	0
0	1	1
1	0	1
1	1	0

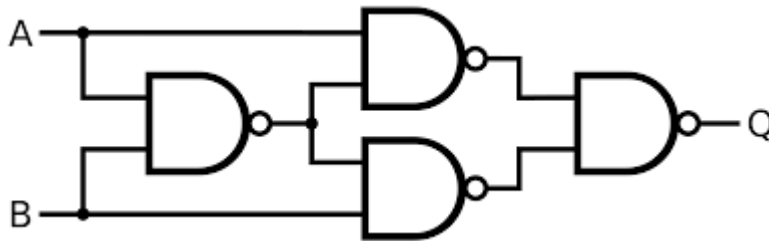

v) X-NOR gate using NAND gate


Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

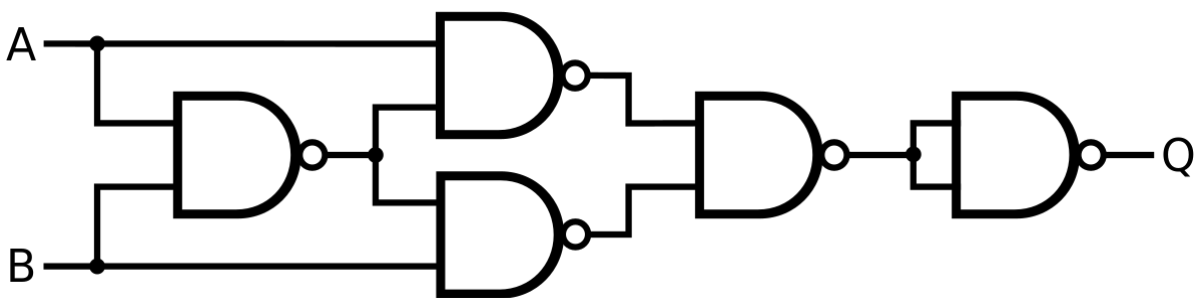

Experiment – 9b


NOR gate using NAND gate:-

INPUT		OUTPUT
A	B	$Q = \overline{A \cdot B}$
0	0	1
0	1	0
1	0	0
1	1	0

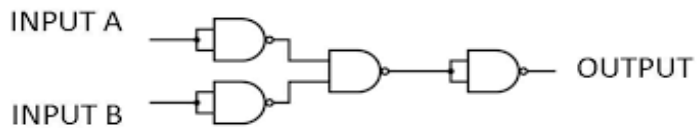


AND gate using NOR gate:-

Input		Output
A	B	$Q = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

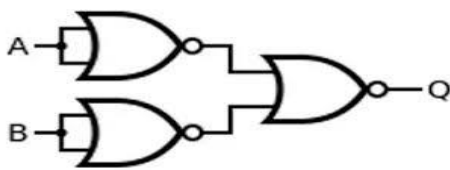

OR gate using NOR gate:-

Input		Output
A	B	$Q = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

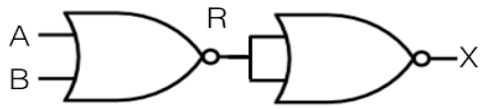


NOT gate using NOR gate:-

INPUT		OUTPUT
A		\bar{A}
0		1
1		0




NAND gate using NOR gate:-

INPUT		OUTPUT
A	B	$Q = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

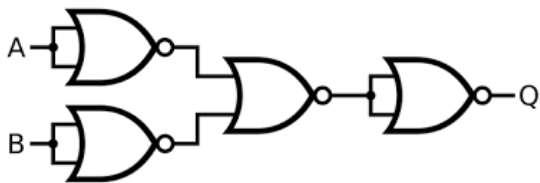


XOR gate using NOR gate:-

INPUTS		OUTPUTS
A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

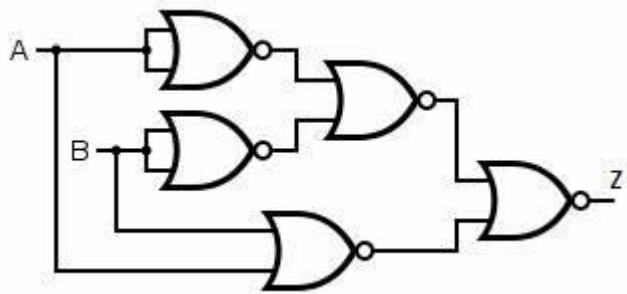

X-NOR gate using NOR gate:-

A	B	A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

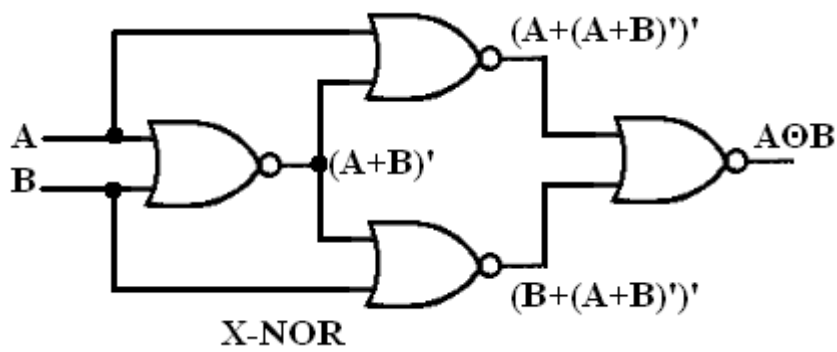

Experiment – 10

AIM OF THE EXPERIMENT

To construct and verify operation of half adder & full adder using logic gates.

APPARATUS REQUIRED

- i. Digital trainer Kit.
- ii. Probes (Connector)
- iii. Power supply.

TRUTH TABLE

Half adder


Input		Output	
A	B	Sum(s)	Carry(c)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full adder

Input			Output	
A	B	C	Sum(s)	Carry(c)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1


Input			Output	
A	B	C	Sum(s)	Carry(c)
1	1	0	0	1
1	1	1	1	1

Logic gate diagram of half adder

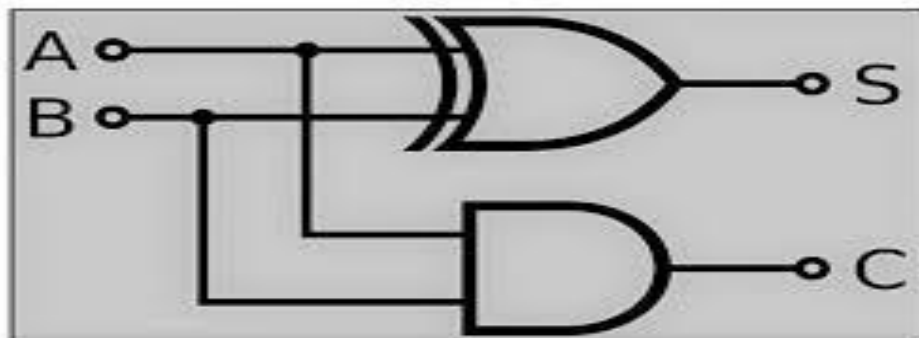

HA Logical Diagram

Logic gate diagram of full adder

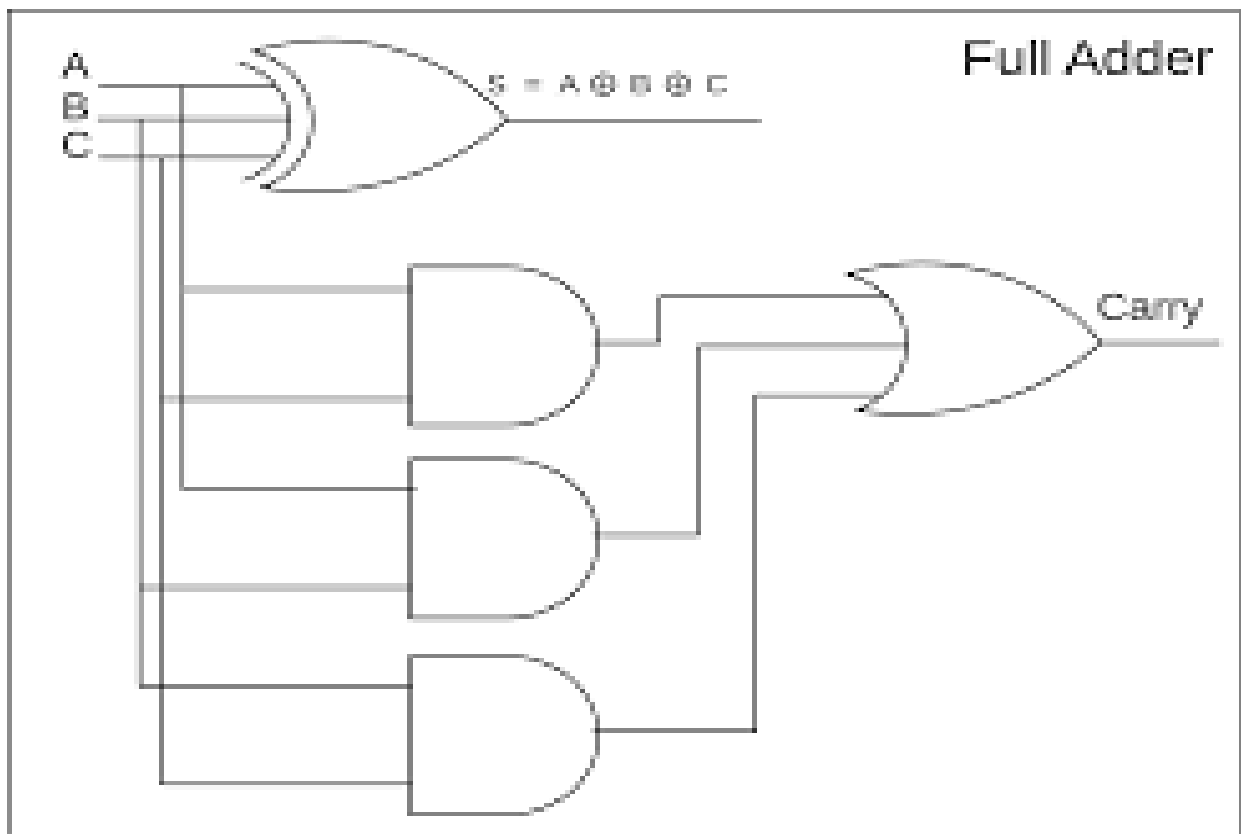

electronicclinic.com

Conclusion

We concluded that the above experiment has been done by as successfully.

Experiment – 11

AIM OF THE EXPERIMENT:-

To design multiplexer (4:2) and Demultiplexer (1:4)

Apparatus required:-

- a. Digital trainer kit
- b. Probes (connector)
- c. Power supply

Truth table:-

Multiplexer (4:1):

SELECTOR		OUTPUT
S ₁	S ₂	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

Demultiplexer (1:4):-

Input selector output

S₁ S₀ D₀ D₁ D₂ D₃

Conclusion:-

We concluded that the above experiment has been done by us successfully.

Experiment – 12

AIM OF THE EXPERIMENT :-

To decide the operation of flip-flop

(i)S-r flip-flop (ii) j-k flip-flop (iii) d- flip-flop (iv) t- flip-flop

Apparatus required:-

- (a)digital trainer kit**
- (b)probas (connector)**
- (c)power supply**


Truth table:-

(i)SR flip flop:-


Input			output
Clk	S	R	Q _{n+1}
0	x	x	Q _n
1	0	0	Q _n
1	0	1	0
1	1	0	1
1	1	1	invalid

(ii)J.K flip flop:-

Input			Output
Clk	J	K	Q Q̄
0	X	X	Memory state
1	0	0	Memory state
1	0	1	0 1
1	1	0	1 0
1	1	1	0 1

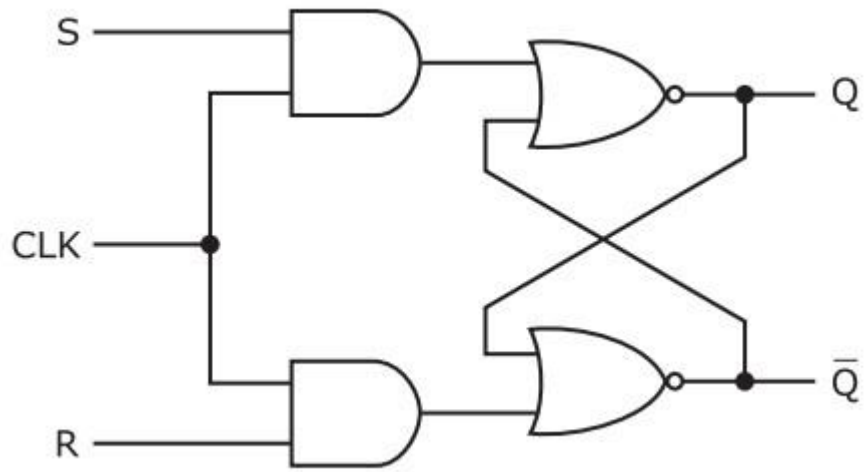
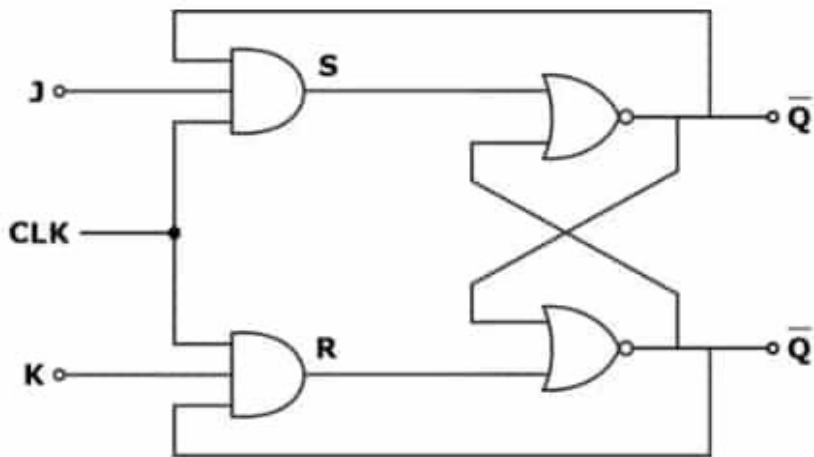
$$S = J\bar{Q} \quad \text{and} \quad R = KQ$$



(iii) d- flip flop :-

Clk	D	Q _{n+1}
0	x	Q _n
1	0	0
1	1	1

(iv) t flip flop:-

Clk	T	Q	\bar{Q}
0	X	Memory state	
1	0	Memory	
1	1	Memory	

Conclusion:-

We concluded that the above experiment has been done by us successfully.