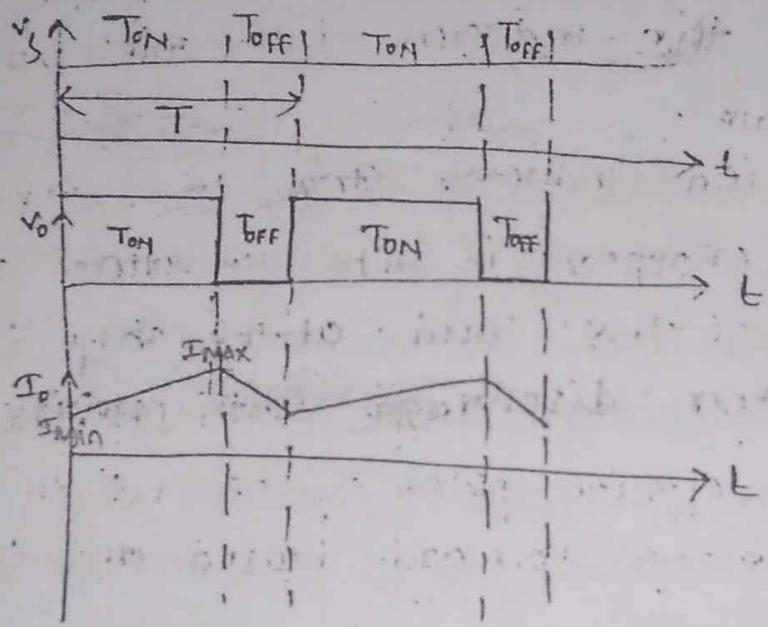
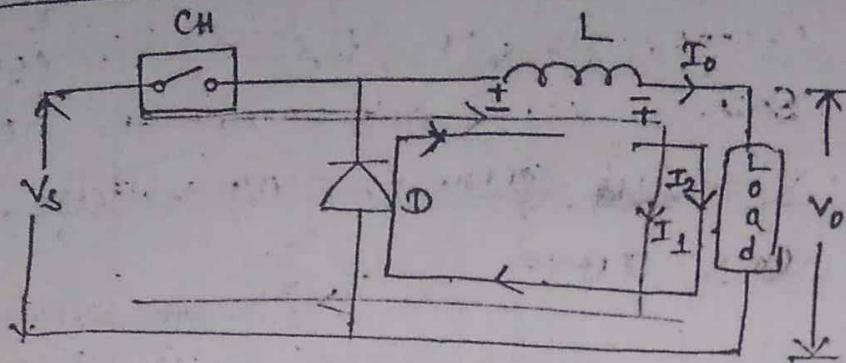


chopper

It is a power electronics device which converts fixed DC to variable DC.

a) step down chopper

b) step up chopper.

Step down chopper

$$v_{o\text{avg}} = v_s \times \left(\frac{T_{on}}{T_{on} + T_{off}} \right)$$

$$= v_s \left(\frac{T_{on}}{T} \right)$$

$$\frac{T_{on}}{T} = D \quad (\text{Duty cycle})$$

$$(D < 1)$$

$$v_{o\text{avg}} = v_s \times D$$

v_s = Supply voltage

Note In this type of choppers

the O/P voltage & current both are +ve.

→ This mode of operation occurs at 1st quadrant and used as Forward Motoring action.


4 < V_s

- It is step down Chopper made of a switch, inductor and diode.
- A chopper is having a controlled switch.
- The load is connected series with load, the source and an inductor.
- When the chopper is ON the load is connected with the source and off current flows through the load and the o/p voltage will appear反相.
- When the current flows through the inductor it changes the inductor from min^m value to max^M value.
- In this period inductor stores the energy.
- When the chopper is OFF o/p voltage will not appear to the load. At the same time the inductor discharge with opposite polarity.
- Due to the opposite polarity of inductor the diode "D" becomes forward biased and starts to conduct.
- Due to this F.B diode a circulating current starts to flow (From L → load → diode - L) which is same in the direction of the previous current and it decreases from max^M value to min^m value.
- The average o/p voltage depends upon the duty cycle ($\delta = \frac{T_{on}}{T}$). The duty cycle is always less than 1 therefore the average o/p voltage (V_{avg}) is

voltage less than the supply voltage, so it is known as a step down chopper.

Step up Chopper

Ap-11-28

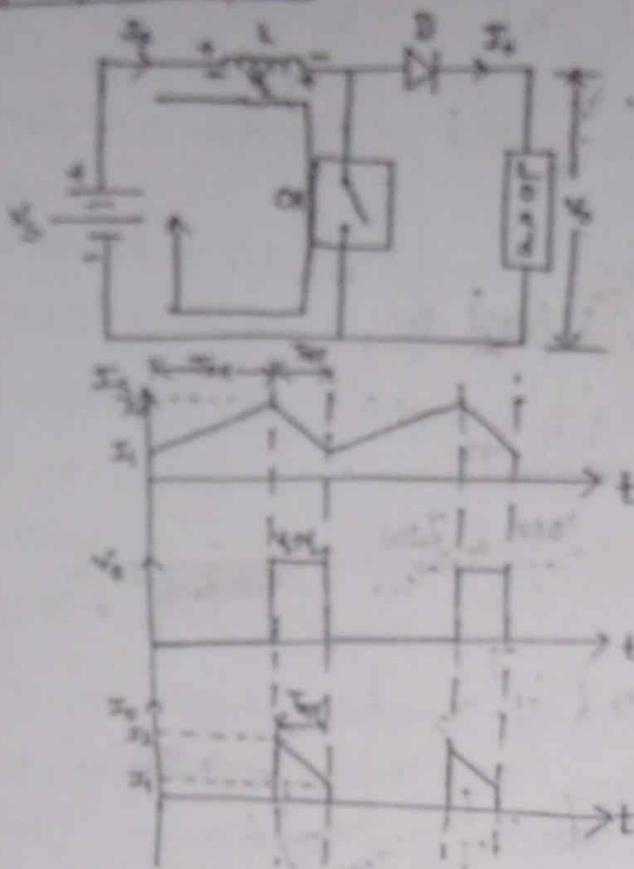


$$\begin{aligned} V_o + V_L - V_s &= 0 \\ \Rightarrow V_o &= V_s + V_L \\ \Rightarrow V_o &= V_s + V_L \end{aligned}$$

Energy stored during T_{ON} .

$$E_{ON} = P_{ON} T_{ON}$$

$$= V_s I_s \times T_{ON}$$
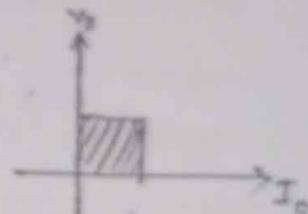
$$= V_s \left(\frac{I_1 + I_2}{2} \right) \times T_{ON}$$



Energy released during T_{OFF} .

$$E_{OFF} = P_{OFF} T_{OFF}$$

$$= (V_o - V_s) \left(\frac{I_1 + I_2}{2} \right) \times T_{OFF}$$

$$\therefore E_{ON} = E_{OFF}$$

$$V_s \left(\frac{I_1 + I_2}{2} \right) \times T_{ON} = (V_o - V_s) \left(\frac{I_1 + I_2}{2} \right) \times T_{OFF}$$

$$\Rightarrow V_s \times T_{ON} = (V_o - V_s) \times T_{OFF}$$

$$\Rightarrow V_s \times T_{ON} = V_o \times T_{OFF} - V_s \times T_{OFF}$$

$$\Rightarrow V_s \times T_{ON} + V_s \times T_{OFF} = V_o \times T_{OFF}$$

$$\Rightarrow v_o(T_{ON} + T_{OFF}) = v_s T_{OFF}$$

$$\Rightarrow v_o = v_s \left(\frac{T_{ON} + T_{OFF}}{T_{OFF}} \right) = v_s \left(\frac{\frac{T}{D}}{T - \frac{T}{D}} \right)$$

$$= v_s \left(\frac{\frac{T}{D}}{\frac{T-D}{D}} + 1 \right)$$

$$= v_s \left(\frac{\frac{T}{D}}{\frac{(T-D)D}{T}} + 1 \right)$$

$$= v_s \left(\frac{\frac{T}{D}}{\frac{T-D}{T}} + 1 \right)$$

$$= v_s \left[\frac{\frac{T}{D}}{\frac{T}{T}} + \frac{\frac{T}{D}}{\frac{T}{T}} + 1 \right]$$

$$\Rightarrow v_o = v_s \left(\frac{\frac{T}{D}}{\frac{T-T}{T}} \right)$$

$$= v_s \left(\frac{\frac{1}{D}}{\frac{T-T}{T}} \right)$$

$$\Rightarrow v_o = v_s \left(\frac{\frac{1}{D}}{1-D} \right) \quad \left(\because \frac{T}{T} = 1 \right)$$

The step up chopper consist of a inductor connected across supply voltage and the load side consist of a Free wheeling diode.

→ when the chopper is on their ~~load~~ is no current flows through the load.

→ At that time the supply current increase from min^m to max^m value.

→ when the chopper is on off voltage does not appear across load.

→ In this period a current is flows ~~from~~. From $v_s \rightarrow L \rightarrow ch \rightarrow v_s$. and inductor stores the energy.

→ when the chopper is OFF o/p voltage appears across load and at that time inductor discharge with opposite polarity.

$$\text{o/p voltage } (V_o) = V_s + V_L$$

→ when the chopper is OFF the diode is forward biased.



→ when the chopper is on there is no current flows through the load and when the chopper is OFF there is a current starts to flow same as o/p current (due to series connection of load and supply) i.e max value to min. value.

→ The o/p voltage depends upon ~~supply voltage~~ duty cycle. duty cycle always less than 1. their o/p voltage is greater than supply voltage. e.g. $V_o = V_s \left(\frac{1}{1-D} \right)$ so it is called step up chopper.

According to direction of current & voltage / quadrant of operation

21.11.20

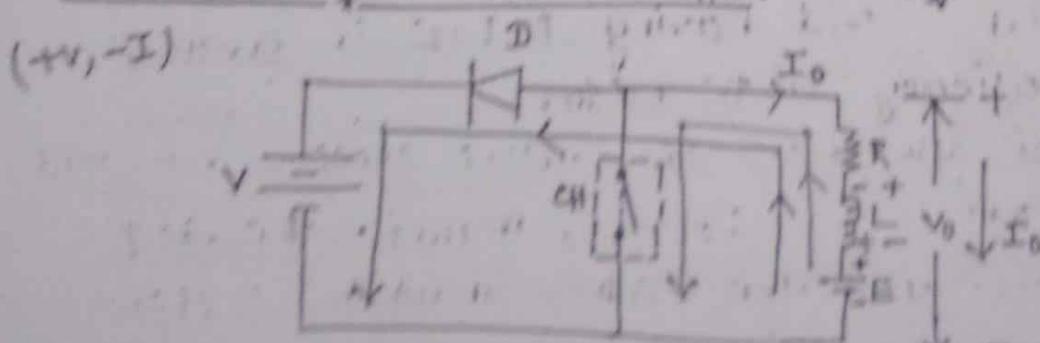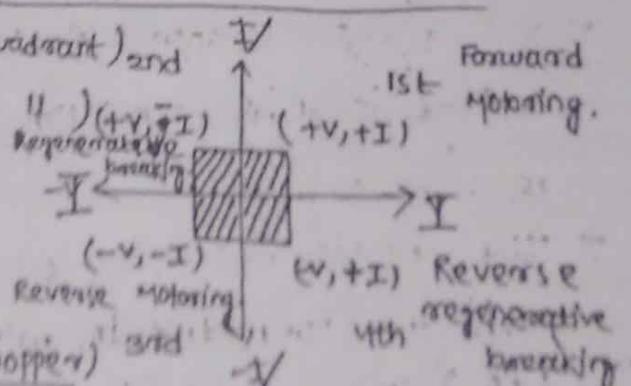- 1) CLASS - A / Type - A (1st quadrant)
 - 2) CLASS - B / Type - B (2nd quadrant)
 - 3) CLASS - C / Type - C
 - 4) CLASS - D / Type - D
 - 5) CLASS - E / Type - E
- Type-B (2nd quadrant chopper)



CH - ON

current flows from the load (E) ($+E \rightarrow L \rightarrow R \rightarrow G \rightarrow -E$)
The current opposite to the o/p current (I_o)

Inductor gets charged

O/P voltage is zero.


CH - OFF

current flows from load to source.

($+E \rightarrow L \rightarrow R \rightarrow D \rightarrow V \rightarrow -E$)

current flows in reverse direction.

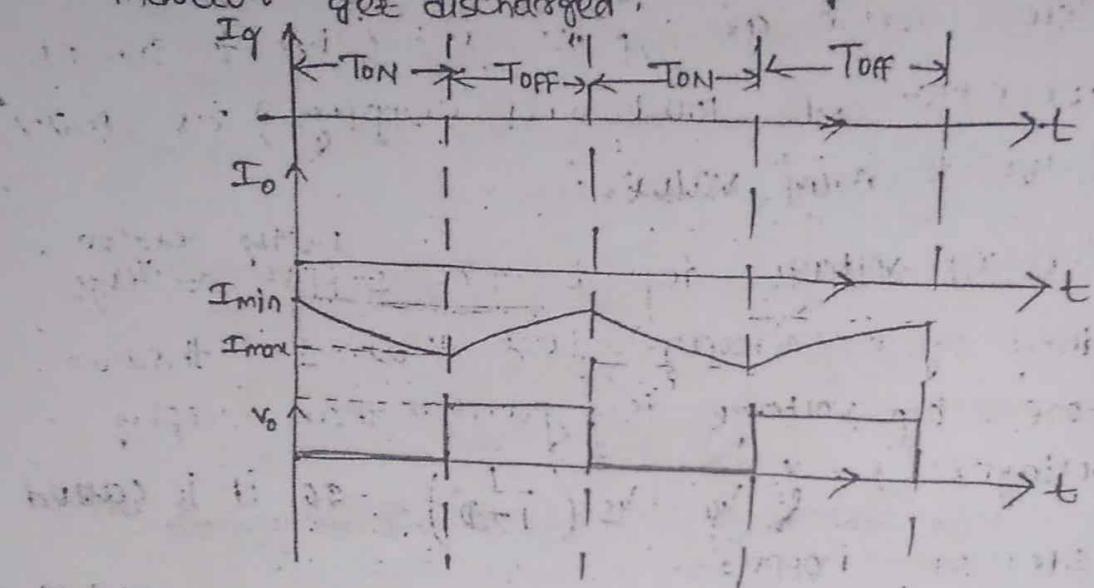O/P voltage is equal to input voltage.
Inductor get discharged.



→ A class-B chopper is also known as a quadrant chopper.

→ In class-B chopper the o/p voltage is +ve and o/p current is -ve.

→ The basic ckt of class-B chopper consists of a diode connected in reverse direction; a chopper (SCR) and a load having R, L, E in series, that is basically a DC motor.

→ The basic operation of class-B chopper explained in 2 mode i.e. Mode-1, in which the chopper (CH) is ON and the Mode-2 in which chopper (CH) is OFF.

Mode-1 (CH-ON)

- As the CH is ON it makes a continuous path i.e.
at the load side through the CH.
- At that time a current starts to flow from
'E' through the CH.
- The current starts to flow from $+E \rightarrow L \rightarrow R \rightarrow D \rightarrow -E$
and changes the inductor from min^m value to
max^M value.
- It is seen that the current is opposite
to the o/p current and taken as -ve.
- As the chopper is ON it makes the o/p short
ckt therefore the o/p voltage is zero.

Mode-2 (CH-OFF)

- When the CH is OFF the inductor starts to
discharge with opposite polarity.
- This makes the diode forward biased.
- A current starts to flow from the load to the
source through diode-D ($+E \rightarrow RL \rightarrow R \rightarrow D \rightarrow V \rightarrow -E$)
- At that time the inductor get discharged and
it is seen that the o/p current flows
in -ve direction.
- As the o/p is directly connected with the source
then the o/p voltage is equal to V_p supply.


From the above two mode of operation
it has been observed that the average
value of o/p voltage is +ve and the average
value of o/p current is -ve.

- As the current flows from load to source
this mode of operation is known as regenerative
breaking.
- This ckt is used to break a dc motor.

Class-C chopper:-

It is the combination of class-A & class-B chopper.

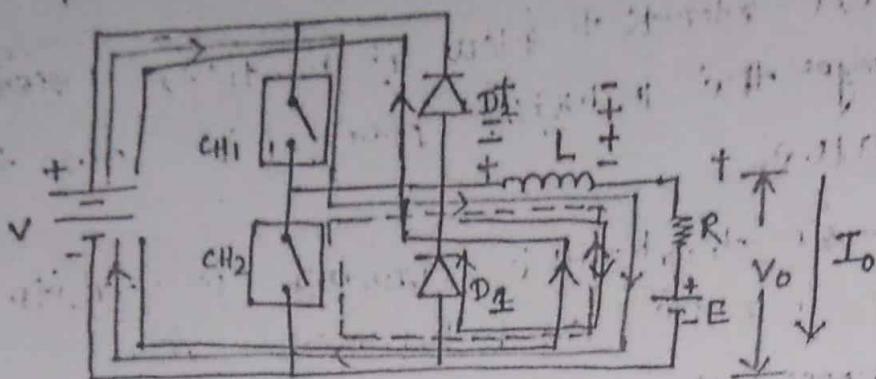- It is also called two quadrant chopper.
- It operates on both 1st & 2nd quadrant.



CH₁ - ON

- * current flows from source to load.
i.e. $V \rightarrow CH_1 \rightarrow L \rightarrow R \rightarrow E \rightarrow V$

* As the current is same as the direction of o/p current, current is +ve.

* The o/p^{voltage} is same as the V_o and +ve.

* The current charges the inductor.

CH₁ - OFF

* Inductor starts to discharge with opposite polarity.

* This makes the diode D₁ forward biased.

* Then a circulating current starts to flow in the closed path i.e. $L^+ \rightarrow R \rightarrow E \rightarrow D_1 \rightarrow L^-$

* As the direction of current is same as the direction of the o/p current, therefore it is taken as +ve.

* The emf is appears at the o/p and is +ve.

* The CH₁ & D₁ used as a class-A chopper.

CH₂ - ON


* A closed path is established at E, R, L & CH₂.


* A current starts to flow from the emf E i.e. $E^+ \rightarrow R \rightarrow L \rightarrow CH_2 \rightarrow E^-$

- * As the current is opposite to the direction of o/p current then, it is taken as -ve.
- * As the current passes through the inductor it charges the inductor in reverse direction.
- * The o/p voltage is +ve.

CH₂-OFF

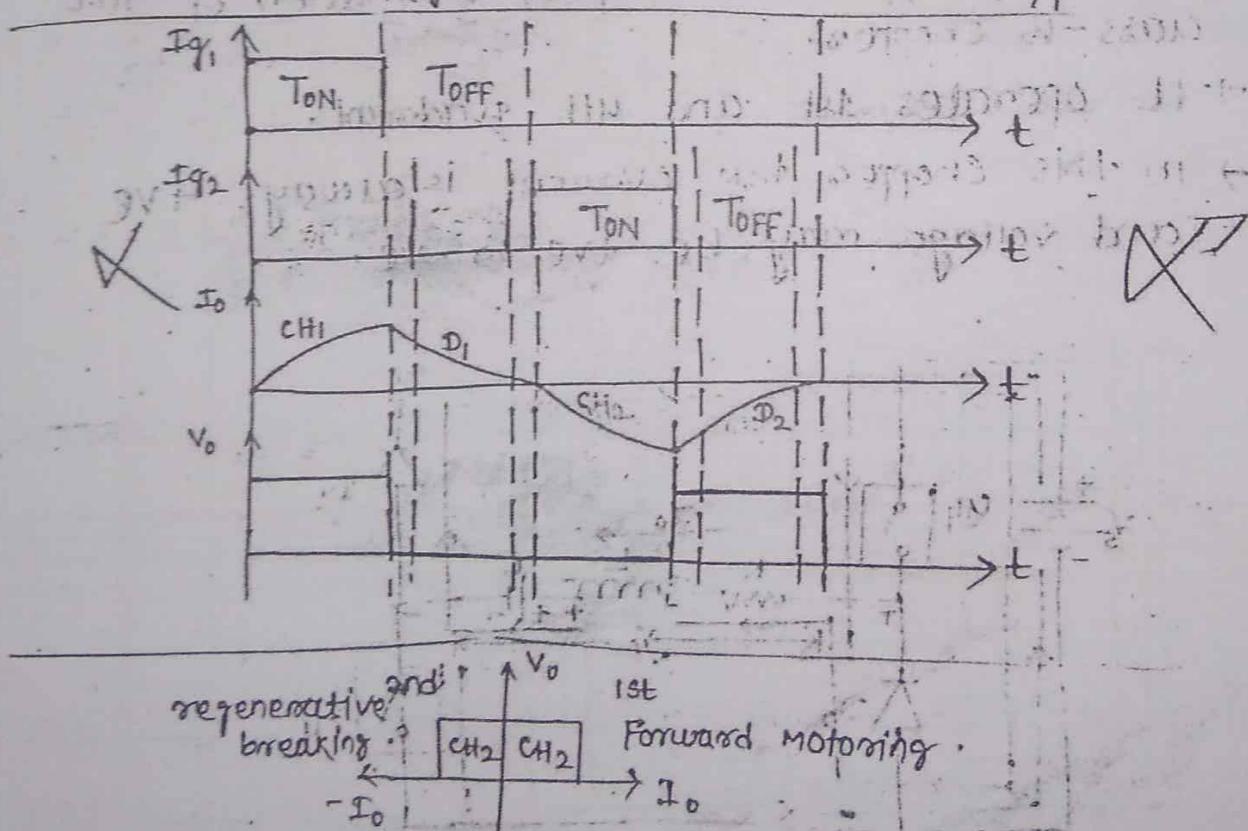- * The inductor starts to discharge with opposite polarity.
- * This makes the diode-D₂ Forward biased.
- * Then a current starts to flow from the Load to source i.e. $L^+ \rightarrow D_2 \rightarrow N \rightarrow E \rightarrow R \rightarrow L^-$.
- * As the current is opposite to the o/p then it is taken as -ve.
- * The o/p voltage is +ve and same as V_p.



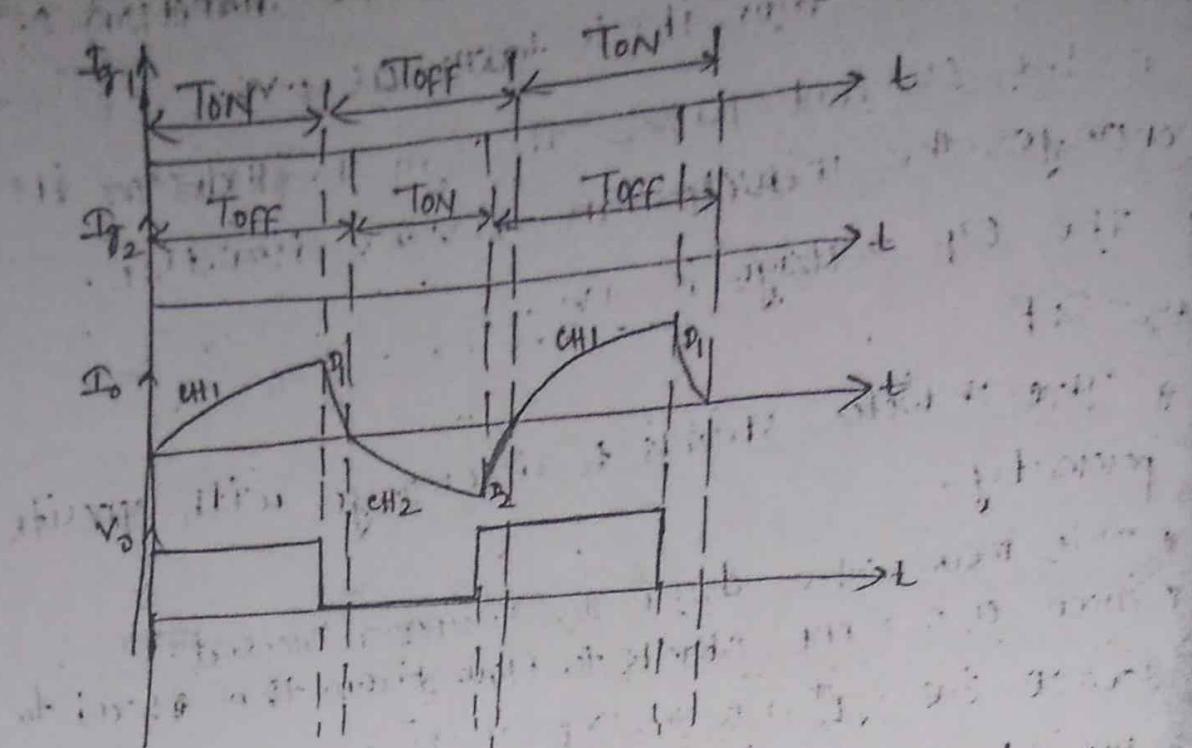


→ class-C chopper, used for forward motoring and regenerative breaking.

class-D chopper:-

It is a two quadrant chopper, combination of two class-B choppers.

→ It operates 1st and 4th quadrant.

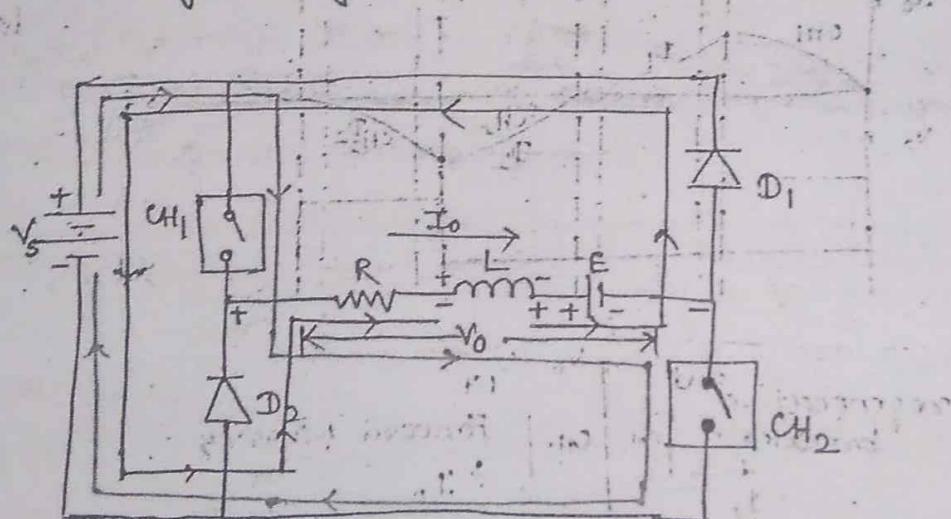→ In this chopper the current is always +ve and voltage may be +ve or -ve.



Mode-1 (Both chopper CH1 & CH2 will ON)


- * Current starts to flow from the source to the load through $V^+ \rightarrow CH_1 \rightarrow R \rightarrow L \rightarrow E \rightarrow CH_2 \rightarrow V^-$.
- * The current charges the inductor.
- * As the direction of the current is same as the o/p

- current then taken as +ve current.
 * the o/p voltage is same as the V_p voltage with +ve polarity.

Mode-2 (Both the Chopper CH₁ & CH₂ will off)

- * inductor discharges with opposite polarity and forward biased diode D₁ & D₂.
 * Then current flows from L \rightarrow E \rightarrow D₁ \rightarrow V \rightarrow D₂ \rightarrow R \rightarrow L.
 * direction of current is same as o/p current then taken as +ve current.

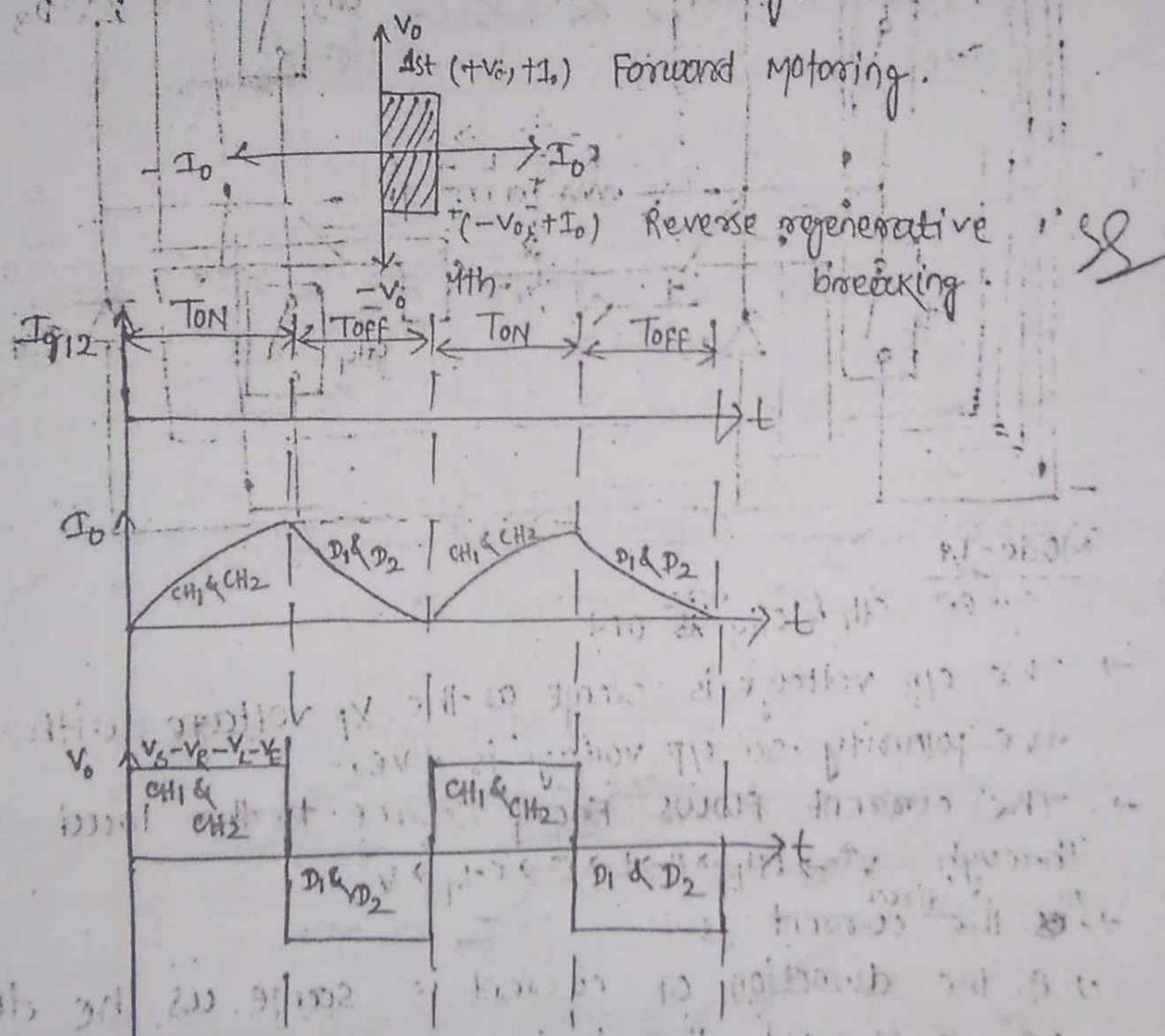
- * The voltage appears across the o/p with opposite polarity so it is taken as -ve voltage.



→ This type of chopper are used for Forward motoring and reverse regenerative breaking.

Class-E chopper:-

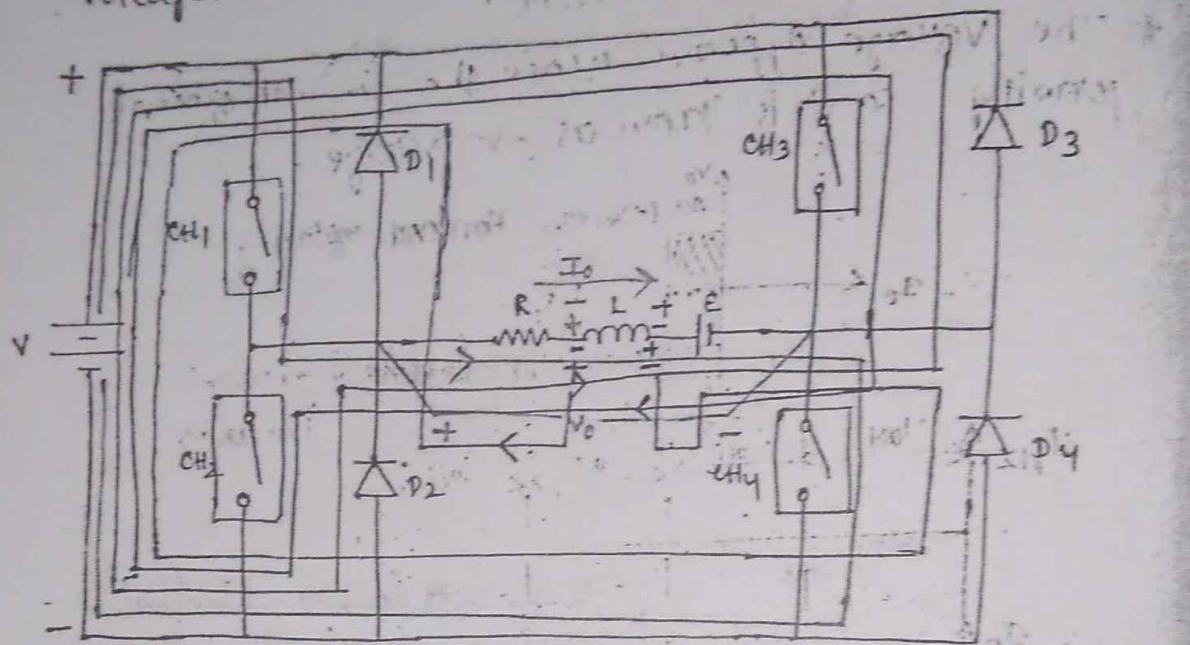- It is a Four quadrant chopper.
- It operates on 1st, 2nd, 3rd & 4th quadrant.
 - It is a parallel connection of two class-E choppers.
 - we can't operate $CH_1 \& CH_2$ and $CH_3 \& CH_4$ simultaneously because it will short the source voltage.



Mode-1

when $CH_1 \& CH_4$ are ON

- The o/p voltage is same as the i/p voltage with +ve polarity so o/p voltage is +ve.
- The current flows from source to the load through $V_i \rightarrow CH_1 \rightarrow R \rightarrow L \rightarrow E \rightarrow CH_4 \rightarrow V_o$.
- As the current is -.
- As the direction of current is same as the direction of o/p current then it is +ve.
- This current charging the inductor.
- As the voltage & current both are +ve then the operation is in 1st quadrant and the mode of operation is known as forward motoring action.

Mode-2

- when C_{H2} & C_{H3} are OFF;
- then the inductor will starts to discharge with opposite polarity.
 - Due to this opposite polarity the diode D_2 & D_3 are forward biased.
 - Due to the Forward biased diode a current starts to flow from $L \rightarrow E \rightarrow D_3 \rightarrow V \rightarrow D_2 \rightarrow R \rightarrow L$.
 - As the direction of current is same as the o/p current it is taken as +ve.
 - As the +ve terminal of source is connected to the -ve terminal of o/p and the -ve terminal of source is connected to the +ve terminal of o/p so the o/p voltage is -ve.
 - As the voltage is -ve & the current is +ve it operates on 4th quadrant and the mode of operation is known as reverse regenerative breaking.

Mode-3

- when C_{H2} & C_{H3} are ON.
- The +ve terminal of the supply voltage connected across the -ve terminal of o/p voltage and viceversa so the voltage is taken as -ve voltage.
 - The current is starts to flow from source to load through $V^+ \rightarrow C_{H3} \rightarrow E \rightarrow L \rightarrow R \rightarrow C_{H2} \rightarrow V^-$.
 - As the direction of current is opposite to the o/p current it is taken as +ve.
 - This reverse current changing the inductor in reverse direction.
 - As the voltage & current both are -ve, it operates on 3rd quadrant and the mode of operation is known as reverse motoring.

Mode - 4

- when C_{H2} & C_{H3} are off
- the inductor starts to discharge with opposite polarity.
 - this makes the diode D_1 & D_2 forward biased.
 - this forward biased diode makes a current flow from $L \rightarrow R \rightarrow D_1 \rightarrow V \rightarrow D_2 \rightarrow E \rightarrow L$.
 - as the direction of current is opposite to the o/p current then it is taken as -ve. and the inductor get discharged.
 - as the +ve terminal of supply is connected to the +ve and -ve terminal is connected to -ve of the o/p voltage then it is taken as +ve.
 - as the voltage is +ve and current is -ve then it operates in 2nd quadrant and the mode of operation is regenerative breaking.

