

# **BHUBANANANDA ORISSA SCHOOL OF ENGINEERING , CUTTACK**



## **DEPARTMENT OF ELECTRONICS AND TELECOMMUNICATION ENGINEERING LAB MANUAL**

Year & Semester: 2Year, 3<sup>rd</sup> Semester

Subject Code /Name: PR-2 , Circuit Theory and Simulation Lab

## **TABLE OF CONTENTS**

<b>SI. No</b>	<b>Name of the Experiment</b>	<b>Pages</b>
1	Measurement of equivalent resistance in series and parallel circuit	3-4
2	Measurement of power and power factor using series R-L-C Load.	5-6
3	Verification of KCL and KVL.	7-10
4	Verification of Super position theorem	11-13
5	Verification of Thevenin"s Theorem	14-15
6	Verification of Norton"s Theorem	16-17
7	Verification of Maximum power transfer Theorem	18-19
8	Determine resonant frequency of series R-L-C circuit.	20
9	Study of Low pass filter & determination of cut-off frequency	21-22
10	Study of High pass filter & determination of cut-off frequency	23-25

# EXPERIMENT NO- 01

**AIM OF THE EXPERIMENT:-** Measurement of equivalent resistance in series and parallel circuit

**COMPONENTS REQUIRED:-**

Sl.No	Name of the Components	Specification	Quantity
1	Resistors	500Ω,680Ω,330Ω,390Ω,270Ω	Each of 2
2	Multi meter	Digital	1
3	Software	Multisim14.1	As required

## **THEORY:-**

### **SERIES CIRCUIT:-**

- In electrical circuit is in series connected the current flowing through the conductor is constant but voltage is not constant and the resistance can be calculated by,

$$R_s = R_1 + R_2 + R_3 + \dots + R_n$$

### **PARALLEL CIRCUIT:-**

- In electrical series is in parallel connected the current flowing through the conductor is not constant but voltage is remain constant and the resistance can be calculated by,

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots + \frac{1}{R_n}$$

### **PROCEDURE:-**

1. Connected the resistors there is to respect circuit diagram.
2. Measured the individual resistance of different resistor with the help of multi meter.
3. Measured the total equivalent resistance as per circuit diagram by multi meter.
4. Compare the observed value and calculation value in both the parallel and series.

### **CALCULATION:-**

Let two resistor are connected in series the n the total or equivalent resistor

is,  $R_1 = 330 \Omega, R_2 = 390 \Omega \quad \rightarrow \quad R_s = R_1 + R_2 = 330 + 390 = 720 \Omega$

If, they are connected in parallel then the equivalent resistance is,

$$R_1 = 330 \Omega, R_2 = 390 \Omega$$

$$\frac{1}{R_P} = \frac{1}{330} + \frac{1}{390} \quad \rightarrow \quad R_P = \frac{330 \times 390}{330 + 390} = 178.8 \Omega$$

### **OBSERVATION TABLE:-**

Sl No	R <sub>1in</sub> (Ω)	R <sub>2in</sub> (Ω)	RESISTANCE IN SERIES		RESISTANCE IN PARALLEL	
			Calculation	Observation	Calculation	Observation
1	500	680	1.18KΩ	1.18KΩ	293.2Ω	288.8Ω
2	270	680	950Ω	958Ω	197.7Ω	193.26Ω
3	330	390	721Ω	720Ω	118.5Ω	178.8Ω

### **CONCLUSION:-**

From the above experiment it we have studied and verified that the observation value is approximately same to the calculation value in both parallel and series circuit.

# EXPERIMENT NO- 02


**AIM OF THE EXPERIMENT** - Measurement of power and power factor using series R-L-C Load.

**APPARATUS REQUIRED:-**

Sl. No	Name of the Equipment	Specification	Quantity
1	Variable Resistor	0-100 $\Omega$	1 no
2	Inductor	40W, 250V	1 no
3	Capacitor	2.5 $\mu$ F	1 no
4	1- $\Phi$ Dimmer Set	0-250v	1 no
5	Voltmeter	0-300v	3 nos
6	Ammeter	0-5A	1 no
7	1- $\Phi$ Wattmeter	250V, 1kW	1 no
8	Power factor Meter	250v, 5A	1 no
9	Connecting Wires	-	As per required

**Theory:-** A series RLC circuit is one the resistor, inductor and capacitor are connected in series across a voltage supply. The resulting circuit is called **series RLC circuit**.

**Circuit Diagram:-**

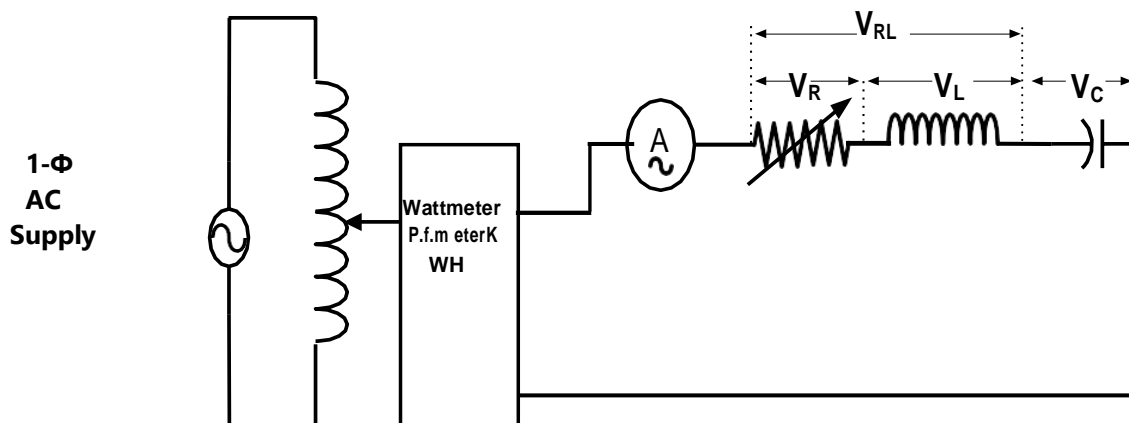

**Observation Table:-**

Sl.no	Type of Load	Reading of Wattmeter	Reading of PF Meter
1	R		
2	L		
3	C		
4	R-L		
5	R-C		
6	L-C		
7	R-L-C		

**Procedure:-**

- 1- We should take all the tools & Instrument for this experiment.
- 2- Connect as per Circuit diagram.
- 3- Then switch ON the supply.
- 4- Take reading of wattmeter and PF meter.

**Conclusion:-**From the above experiment , we learnt about the measurement of power and power factor using series R-L-C Load.

# EXPERIMENTNO-03

**AIM OF THE EXPERIMENT:-**Verification of KCL&KVL.

**EQUIPMENT REQUIRED:-**

SI No	Name of the Components	Specification	Quantity
1	Verification Kit	(OMEGA-ETB-201)	1
2	Patch Cord	-----	As per required
3	Power Supply	0-12Volt	-----
4	Multi meter	Digital meter	1

**THEORY:-**

- KCL states that the algebraic sum of all the current meeting at a point or junction is equal to zero.
- It can be stated that total in coming current at a point will be equal to the total out going current.
- For verification of KCL we consider the given circuit.

**PROCEDURE: -**

1. Connect the circuit as per the circuit diagram.
2. Vary the voltage to take 5 different reading.
3. Observe different ammeter reading for each input voltage.
4. Compare the reading with the total current following the ckt.

**CALCULATION:-**

$$R_1 = 270\Omega \quad R_2 = 330\Omega$$

$$R_3 = 500\Omega \quad V = 9V$$

$$R_{eq} = (270 \parallel 330) + 500$$

$$= 148.5 + 500 = 648.5\Omega$$

$$I_3 = \frac{V}{R_{eq}} = \frac{9}{648.5} = 0.013A = 13mA$$

$$I_1 = \frac{(0.013) \times 330}{270 + 330} = 7.15mA$$

$$I_2 = \frac{(0.013) \times 270}{270 + 330} = 5.85mA$$

$$\rightarrow I_1 + I_2 = 7.15mA + 5.85mA = 13mA$$

**OBSERBATIONTABLE:-**

<b>Sl No</b>	<b>Input voltage</b>	<b>I<sub>1</sub>(270Ω) In mA</b>	<b>I<sub>2</sub>(330Ω) In mA</b>	<b>I<sub>3</sub>(500Ω) In mA</b>	<b>I<sub>1</sub>+I<sub>2</sub> in mA</b>
<b>1.</b>	10V	8.53	6.95	15.49	15.48
<b>2.</b>	9V	7.60	6.2	13.9	13.8
<b>3.</b>	8V	6.84	5.58	12.44	12.42
<b>4.</b>	7V	6	4.89	10.91	10.89
<b>5.</b>	5V	4.30	3.51	7.82	7.81



# KIRCHHOFF'S VOLTAGE LAW

## THEORY:-

- KVL states that the algebraic sum of 'EMF' and product of current and resistance in a closed loop is equal to zero.
- For the verification of this theorem we have taken a circuit as shown in the figure.
- In the given circuit we have one 'EMF' and two resistance value  $270 \Omega$  and  $330 \Omega$ .
- The voltage across  $270 \Omega$  resistor is taken ' $V_1$ ' and across  $330 \Omega$  resistor is taken ' $V_2$ '.

## PROCEDURE: -

1. Connect circuit as per the circuit diagram.
2. Give the power apply to the circuit.
3. Now the measure the voltage across each resistor using Multi meter and note down the observe value in the observation table.
4. Now add all the three values of voltage obtain and compare it with the emf value.
5. This procedure may be respected for variable voltage values.

## CALCULATION:-

Theoretically applying KVL to the given circuit,  $V - IR_1 - IR_2 = 0$

$$\Rightarrow 9 - I \times 270 \Omega - I \times 330 \Omega = 0$$

$$\Rightarrow 9 - I \times (270 + 330) = 0$$

$$\Rightarrow 9 = I \times (270 + 330)$$

$$\rightarrow I = \frac{9}{270+330} = 0.015A \rightarrow$$

$I = 15mA$
------------

### **OBSERBATIONTABLE:-**

<b>SINo</b>	<b>V<sub>1</sub>(270 Ω)</b>	<b>V<sub>2</sub>(330 Ω)</b>	<b>V<sub>t</sub>( V<sub>1</sub>+V<sub>2</sub>)</b>	<b>TotalEMFApplied</b>
<b>1</b>	4.57	5.70	10.27	10V
<b>2</b>	3.98	4.88	8.86	9V
<b>3</b>	3.22	3.91	7.13	7V
<b>4</b>	2.30	2.80	5.10	5V
<b>5</b>	0.90	1.10	2.00	2V

### **CONCLUSION:-**

From the above experiment we observe that sum of emf and voltage drop is equal to zero.

# **EXPERIMENTNO-04**

## **SUPERPOSITION THEOREM**

**AIM OF THE EXPERIMENT:-**Verification of Super position theorem

**EQUIPMENT REQUIRED:-**

<b>SL. NO</b>	<b>NAMEOF THE COMPONENT</b>	<b>SPECIFICATION</b>	<b>QUANTITY</b>
<b>01</b>	VERIFICATIONKIT	OMEGA TYPE-ETB201	01
<b>02</b>	POWERSUPPLY	0-12V	-
<b>03</b>	PATCHCORDS	-	As required
<b>04</b>	MULTIMETER	-	-

**THEORY:-**

In any linear bilateral network containing two or more independent sources (voltage or current sources or combination of voltage and current sources), the resultant current / voltage in any branch is the algebraic sum of currents / voltages caused by each independent source acting along, with all other independent sources being replaced meanwhile by their respective internal resistances.

The voltage source replaced by short circuit and the current circuit replaced by open circuit. The voltage source replaced by short the resistances of the source are replaced at the time of source elimination.

If the current produced by one source is in one direction while that produced by the other is in the opposite direction through the same resistor, the resulting current is the difference of the two and has the direction of the larger current. If the individual currents are in the same direction, the resulting current is the sum of two and has the direction of either current..

The total power delivered to a resistive element must be determined using the total current through or the total voltage across the element and cannot be determined by a simple sum of the power levels established by each source.

## **PROCEDURE: -**

- Connect the power supply to the verification kit.
- Make the connection as per the circuit diagram.
- Remove  $V_2$  and close the circuit through a patch cord.
- Measure  $I_{31}$  in the ammeter.
- Now put  $V_2$  in the circuit and remove  $V_1$  from the circuit. Close the circuit through a patch cord in place of  $V_1$ .
- Now replace and measure  $I_{32}$  in the ammeter.
- Now replace  $V_1$  and switch on both the sources.

## **CALCULATION:-**

Now eliminate the  $V_2$  Voltage from the circuit,  $R_{eq} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$

Due to voltage source  $V_1$ ,  $I_{31} = I_1 \times \frac{R_2}{R_2 + R_3} = \frac{V_1}{R_{eq}} \times \frac{R_2}{R_2 + R_3}$

Now eliminate the  $V_1$  voltage source from the circuit,  $R_{eq} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$

Due to voltage source  $V_2$ ,  $I_{32} = I_2 \times \frac{R_1}{R_1 + R_3} = \frac{V_2}{R_{eq}} \times \frac{R_1}{R_1 + R_3}$

$$\text{So, } V_1 = 9 \text{ V, } V_2 = 5 \text{ V, } R_1 = 270 \Omega, \quad R_2 = 330 \Omega, \quad R_3 = 390 \Omega,$$

$$R'_{eq} = 448.75 \Omega, \quad R''_{eq} = 489.54$$

$$\text{So, } I_{31} = \frac{9}{448.75} \times \frac{330}{330+390} = 9.19 \text{ mA}$$

$$\text{Similarly, } I_{32} = \frac{5}{489.54} \times \frac{270}{270+390}$$

$$I_3 = I_{31} + I_{32} = 9.19 + 4.17 = \mathbf{13.36 \text{ mA}}$$

$$\text{Loop-1, } 9 - 270I_1 - (I_1 - I_2) 390 = 0$$

$$9 - 270I_1 - 390I_1 + 390I_2 = 0$$

$$\Rightarrow 660I_1 - 390I_2 = 9 \dots\dots\dots (i)$$

$$\text{Loop-2, } -330I_2 - 5 - (I_2 - I_1) 390 = 0$$

$$\Rightarrow -330I_2 - 5 - 390I_2 + 390I_1 = 0$$

$$\Rightarrow 390I_1 - 720I_2 = 5 \dots\dots\dots (ii)$$

Now solving the equations (i) and (ii) we get,

$$I_1 = 0.014 = 14 \text{ m A} \quad , \quad I_2 = 6.5 \times 10^{-4} = 0.65 \text{ mA So}$$

$$, I = I_1 - I_2 = 14 - 0.65 = 13.35 \text{ m A}$$

**TABULATION:-**

Sl No.	V <sub>1</sub> (Volt)	V <sub>2</sub> (Volt)	Total I <sub>3</sub> where both (V <sub>1</sub> ) and (V <sub>2</sub> ) active	Current where (V <sub>1</sub> ) active I <sub>31</sub>	Current where (V <sub>2</sub> ) active I <sub>32</sub>	Total (I = I <sub>31</sub> + I <sub>32</sub> )
01	9	5	13.04	8.97	4.09	13.06
02	9	7	14.65	8.97	5.65	14.26
03	9	9	16.29	8.97	7.30	16.27
04	9	10	17.28	8.97	8.12	17.09
05	9	11	17.98	8.97	8.97	17.64

**CONCLUSION:-**

From the above experiment we studied and observed that different branch current of the circuit using Super position theorem.

# **EXPERIMENTNO-05**

## **VERIFICATION OF THEVENIN'S THEORM**

**AIM OF THE EXPERIMENT:-**Verification of Thevenin's Theorem.

### **EQUIPMENTSREQUIRED**

SI No	Name of the Components	Specification	Quantity
1	Resistors	500Ω,680Ω,330Ω,270Ω	As Required
2	Multi meter	Digital	1
3	Connecting wire	-----	-----
4	DC power supply	-----	-----

### **THEORY**

Any linear active 2 terminal n/w consisting in of voltage and current source with some resistance. It can be replaced by an equivalent Thevenin's voltage source or voltage source having its value equal to the Thevenin's equivalent voltage with a series resistor which is known as Thevenin's resistance. The equivalent voltage source is represented by ' $V_{th}$ ' and equivalent resistance is represented by ' $R_{th}$ '. To find the Thevenin's equivalent voltage first we have to open circuit the load terminals. The open circuited voltage  $V_{AB}$  is the required Thevenin's voltage. We have again equal to the voltage across the point 'P' and 'Q' so  $V_{PQ}=V_{AB}=V_{TH}$ .

### **PROCEDURE**

1. Start–Electronics workbench –Multisim14.1
2. Select the component from place Component library according to given circuit diagram.
3. Connect the multi meter.
4. Make connection as per a circuit diagram.
5. Simulate Run.
6. Double click to the multi meter.
7. See the output result.

### **CALCULATION**

$$R_1=300\text{Ohm}, R_2=500\text{Ohm}, R_3=680\text{Ohm}, R_L=9\text{v}$$

### **STEP-1**

Calculate the  $V_{th}$  across load AB terminal and open the 270 ohm resistor.

$$V_s = IR_1 + IR_2 = I(R_1 + R_2)$$

$$I = V_s / (R_1 + R_2) = 9 / (330 + 500) = 1.08 \text{ mA}$$

$$V_{th} = V_{AB} = I \times 500 = 1.08 \times 500 = 5.42 \text{ V}$$

### **STEP-2**

Calculate the  $R_{th}$  across AB terminal by short circuit the voltage source.

$$R_{ab} = (330 \parallel 500) + 680 = \frac{330 \times 500}{330 + 500} + 680 = 878.795 \text{ Ohm}$$

Then find  $I_{th}$  in the Thevenin's equivalent circuit,

$$I_{th} = \frac{V_{th}}{R_{th} + R_L} = \frac{5.422}{878.795 + 270} = 4.71 \text{ mA}$$

$I_L$  in find I will be equal to the I in thevenin's equivalent circuit.

### **TABULATION**

#### **CALCULATED TABLE:-**

Sl No.	Applied voltage in V	$V_{th}$ In Volt	$R_{th}$ in ohm	$I_L$ In mA
01	09	5.42	878.795	4.72

#### **OBSERVATION TABLE:-**

Sl. No	Applied voltage in volt	$V_{th}$ in volt	$R_{th}$ in ohm	$I_L$ In mA
01	07	4.217	878.795	3.671
02	08	4.819	878.795	4.195
03	09	5.422	878.795	4.72
04	10	6.020	878.795	5.244
05	11	6.627	878.795	5.768
06	12	7.229	878.795	6.293

### **CONCLUSION**

From the above experiment we know that how to verify Thevenin's theorem by using multisim14.1.

# EXPERIMENTNO-06

## VERIFICATION OF NORTON'S THEOREM

AIM OF THE EXPERIMENT:-Verification of Norton's Theorem.

### COMPONENT REQUIRED:-

Sl No	Name of the Components	Specification
1	Software	Multisim-14.1
2	Resistors	500Ω,680Ω,330Ω,270Ω
3	DC Power source	7Volt
4	Multi meter	As required

### THEORY:-

- In any linear bilateral network containing one or more voltage sources can be replaced by an equivalent circuit.
- Consisting of current  $[I_N]$  in parallel with the equivalent resistance.
- $I_N$  is the short circuited current following through the load terminals.

### PROCEDURE:-

1. Start → Electronics work bench → Multisim 14.1.
2. Select component from place → Component library according to following circuit.
3. Connect the multi meter.
4. Make connection according.
5. Simulate → Run
6. Double click on the multi meter.
7. See the output result.

### CALCULATION:-

#### STEP-1

First draws the given original circuit.

#### STEP-2

Assume load resistance as short circuited and calculate Norton's equivalent current as short circuited path.

$$\begin{aligned} \text{Apply mesh analysis, in loop 1 we get, } & \rightarrow 7 - 330I_1 - 500I_1 + 500I_2 = 0 \\ \rightarrow 7 - 830I_1 + 500I_2 = 0 & \quad \rightarrow 830I_1 - 500I_2 = 7 \text{ -----(1)} \end{aligned}$$

$$\begin{aligned} \text{Apply mesh analysis, in loop 2 we get, } & \rightarrow -500I_2 + 500I_1 - 680I_2 = 0 \\ \rightarrow -1180I_2 + 500I_1 = 0 & \quad \rightarrow 500I_1 - 1180I_2 = 0 \text{ -----(2)} \end{aligned}$$

By comparing or calculating Eq.1 & Eq.2 we get,  $I_1 = 0.011 \text{ A} = 11 \text{ mA}$  &  $I_2 = 4.79 \text{ mA}$



So, current across short circuit path or  
Norton's equivalent current  $[I_N]=4.79\text{mA}$

**STEP - 3**

Assume load resistance as open circuit and  
find equivalent resistance or Norton's  
equivalent resistance,

$$R_N=(330 \parallel 500)+680$$

$$=198.795+680=878.795\Omega$$

**STEP-4**

Now draw Norton's equivalent circuit and find  
current across load resistance.

$$I_L = \frac{4.79 \times 10^{-3} \times 878.795}{878.795 + 270} = 3.66\text{mA}$$

**TABULATION:-**

**Calculated Tabulation: -**

SI No	Applied voltage in (V)	$I_N$ in (mA)	$R_N$ in(mA)	$I_L$ in(mA)
1	7V	4.798	878.795	3.67

**Observation Tabulation:-**

SI No	Applied Voltage in(V)	$I_N$ in (mA)	$R_N$ in (mA)	$I_L$ in (mA)
1	7	4.798	878.795	3.670
2	8	5.484	878.795	4.195
3	9	6.169	878.795	4.719
4	10	6.855	878.795	5.244
5	11	7.540	878.795	5.768
6	12	8.226	878.795	6.293

**CONCLUSION:-**

From the above experiment we know that how to verify the Norton's theorem by  
using software Multisim 14.1.

-

# EXPERIMENTNO-07

## VERIFICATION OF MAXIMUM POWER TRANSFER THEOREM

**AIM OF THE EXPERIMENT:-** To study & verify Maximum power transfer theorem.

### COMPONENT REQUIRED:-

SI No	Name of the Components	Specification
1	Software	Multisim-14.1
2	Resistors	1KΩ
3	Variable Resistor	10KΩ
4	DC Power source	12Volt
5	Multi meter	As required
6	Voltmeter	As required

### THEORY:-

A resistive load being connected to a DC network receives maximum power when the load resistance is equal to the internal resistance of the source network as seen from load end.

### EXPLANATION:-

A variable resistance ' $R_L$ ' is connected to a dc source network where ' $V_0$ ' represent the Thevenin's Voltage and ' $R_{th}$ ' represent the Thevenin's resistance of the source network. We have to find out the value of ' $R_L$ ' such that it receives the maximum from the dc source with reference to the fig the following can be written.

The current through the network ' $I_0$ ' will be equal to mean ,  $I_0 = \frac{V_0}{R_{TH} + R_L}$

$I_0$

The power delivered to the resistive load,  $P_L = [I_0]^2 R_L = \frac{V_0^2 R_L}{(R_{TH} + R_L)^2}$

$P_L$  can be maximized by varying the  $R_L$  & hence maximum power ( $P_{max}$ ) can be delivered

when,  $\frac{dP_L}{dR_L} = 0$

$$\Rightarrow \frac{d}{dR_L} \left[ \frac{V_0^2 R_L}{(R_{TH} + R_L)^2} \right] = 0 \Rightarrow V_0^2 \frac{d}{dR_L} \left[ \frac{R_L}{(R_{TH} + R_L)^2} \right] = 0 \Rightarrow V_0^2 \frac{(R_{TH} + R_L)^2 \cdot 1 - R_L \cdot 2(R_{TH} + R_L)}{(R_{TH} + R_L)^4} = 0$$

$$\Rightarrow \frac{V_0^2}{(R_{TH} + R_L)^4} (R_{TH} + R_L)^2 - \frac{2R_L}{(R_{TH} + R_L)^3} = 0 \Rightarrow (R_{TH} + R_L) [(R_{TH} + R_L) - 2R_L] = 0$$

$$\Rightarrow R_{TH} + R_L - 2R_L = 0 \Rightarrow R_{TH} - R_L = 0 \Rightarrow R_{TH} = R_L \Rightarrow \text{Thus } P_L = \frac{V_0^2 R_L}{(R_{TH} + R_L)^2}$$

By replacing  $R_{TH} = R_L$  in this equation,  $P_L = \frac{V_0^2 R_L}{(2R_L)^2} \Rightarrow P_L = \frac{V_0^2}{4R_L} \Rightarrow P_{max} = \frac{V_0^2}{4R_L}$

### PROCEDURE:-

- 1) Start → Electronicsworkbench → Multisim14.1.
- 2) Select component from place → Component library according to following circuit.
- 3) Connect the multi meter.
- 4) Make connection according.

- 5) Simulate → Run
- 6) Double click on the multi meter.
- 7) See the output result

**CALCULATION:-**

**STEP-1**

First draws the given original circuit.

**STEP-2**

Assume load resistance as open circuited & calculate Thevenin's equivalent voltage as short circuited path

Apply mesh analysis, in loop we get,

$$12 - 1000I_1 - 1000I_1 = 0 \rightarrow 12 - 2000I_1 = 0$$

$$2000I_1 = 12 \rightarrow I_1 = 6\text{mA}$$

So, voltage across open circuit path or Thevenin's equivalent voltage  $[V_{TH}] = 6\text{V}$

**STEP-3**

Assume load resistance as open circuit and find

Thevenin's equivalent resistance,

$$R_{TH} = (1000 \parallel 1000) + 1000 = 500 + 1000 = 1500\Omega \rightarrow R_{TH} = 1.5\text{K}\Omega$$

**STEP-4**

After Thevenin's equivalent resistance found the  $P_{max}$  or maximum power of the circuit,

$$P_{max} = \frac{V^2}{4R_L} = \frac{6^2}{4 \times 1500} = 6\text{mW}$$

**TABULATION**

**GRAPH**

Sl No	Load resistance (RL) (5KΩ)	V <sub>RL</sub> in (V)	Po(V <sub>RL</sub> /RL) In mW
1	500(10%)	1.5	4.500
2	1000(20%)	2.4	5.760
3	1500(30%)	3.0	6.000
4	2000(40%)	3.4	5.870
5	2500(50%)	3.7	5.625

**CONCLUSION:-**

From the above experiment we concluded that for  $R_L = R_{th}$  we get the maximum power transferred to the load end by using Multisim 14.1.

# **EXPERIMENTNO-08**

## **RESONANCE CIRCUIT**

**AIM OF THE EXPERIMENT**:-Determine resonant frequency of series R-L-C circuit

**COMPONENT REQUIRED:-**

SI No	Name of the Components	Specification
1	Software	Multisim-14.1
2	Resistors	40kΩ
3	Capacitor	30mF
3	Inductor	0.1mH
4	Sine wave function generator	1kHz,1Vpk

**THEORY:-**

**SERIES RESONANCE:-**

When an inductor and capacitor are connected in series the output current or voltage are maximum at a particular frequency depending on the values of inductor and capacitor.

This is called as resonance condition and the frequency is called resonating frequency at which the circuit attains resonance.

For a series L-C Resonant is given by,  $F_0 = \frac{1}{2\pi\sqrt{LC}}$


$$F_0 = \frac{1}{2\pi\sqrt{LC}}$$

**PROCEDURE:-**

- 1) Start–ElectronicsWorkbench–Multisim14.1.
- 2) Select the components from place – Components library according to the following circuit
- 3) ConnectthePowersource[simulate–instrument-Powersource(A.CBattery)]
- 4) Simulate-Run

 **CONCLUSION:-**

The circuit at resonance at particular frequency the frequency at which the amplitude get increased.





# **EXPERIMENTNO-09**

## **LOW-PASSFILTER**

**AIM OF THE EXPERIMENT**:-Study of Low pass filter & determination of cut-off frequency.

### **COMPONENT REQUIRED**:-

SI No	Name of the Components	Specification
1	Software	Multisim-14.1
2	Resistors	1k $\Omega$
3	Capacitor	1 $\mu$ F
3	Sine wave function generator	1kHz,1Vpk
4	Bode Plotter	As required

### **THEORY**:-

A low-pass filter is a filter that passes low- frequency signals but attenuates (reduces the amplitude of) signals with frequencies higher than the cutoff frequency.

The actual amount of attenuation for each frequency varies from filter to filter.

It is sometimes called a high-cut filter, or treble cut filter when used in audio applications.

A low-pass filter is the opposite of a high-pass filter , and a band- pass filter is a combination of a low-pass and a high-pass.

Low-pass filters exist in many different forms, including electronic circuits (such as a hiss filter used in audio), digital filters for smoothing sets of data, acoustic barriers, blurring of images, and so on.

The moving average operation used in fields such as finance is a particular kind of low-pass filter, and can be analyzed with the same signal processing techniques as are used for other low-pass filters.

Low-pass filters provide a smoother form of a signal, removing the short-term fluctuations, and leaving the longer-term trend.

In an electronic low-pass RC filter for voltage signals, high frequencies contained in the input signal are attenuated but the filter has little attenuation below its cutoff frequency which is  $f_c = \frac{1}{2\pi RC}$  determined by its RC time constant.

$$f_c = \frac{1}{2\pi RC}$$

### **PROCEDURE:-**

1. Start–Electronics Workbench–Multisim14.1.
2. Select the components from place–Components library according to following circuit.
3. Connect the Bode Plotter [Simulate–Instrument-Bode Plotter].
4. Simulate-Run.
5. Double click on Bode Plotter.

### **OBSERVATION:-**

In the above experiment we observe that the output of CRO is much difference when the theoretical characteristic curve and the practical and theoretical curve are different.

### **CONCLUSION:-**

From the above experiment we studied those characteristics of Low pass Filter by using software Multisim14.1.



## EXPERIMENT NO –10

### AIM OF THE EXPERIMENT


Study of High pass filter & determination of cut-off frequency

### EQUIPMENT REQUIRED


SINo	Name of the Components	Specification
1	Software	Multisim-14.1
2	Resistors	1k $\Omega$
3	Capacitor	1 $\mu$ F
3	Sine wave function generator	1kHz, 1Vpk
4	Bode Plotter	As required

### THEORY


The High Pass Filter Circuit

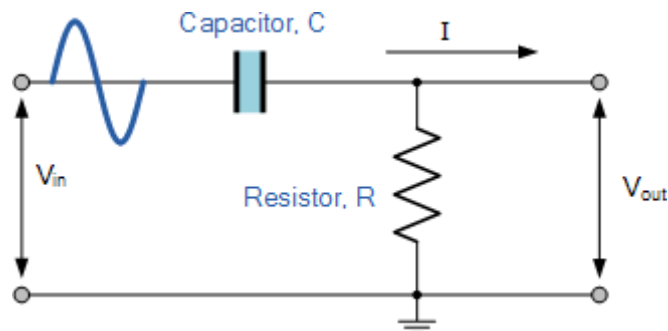

In this circuit arrangement, the reactance of the capacitor is very high at low frequencies so the capacitor acts like an open circuit and blocks any input signals at  $V_{IN}$  until the cut-off frequency point ( $f_c$ ) is reached. Above this cut-off frequency point the reactance of the capacitor has reduced sufficiently so it now acts more like a short circuit allowing all of the input signal to pass directly to the output as shown below in the filter's response curve.

 

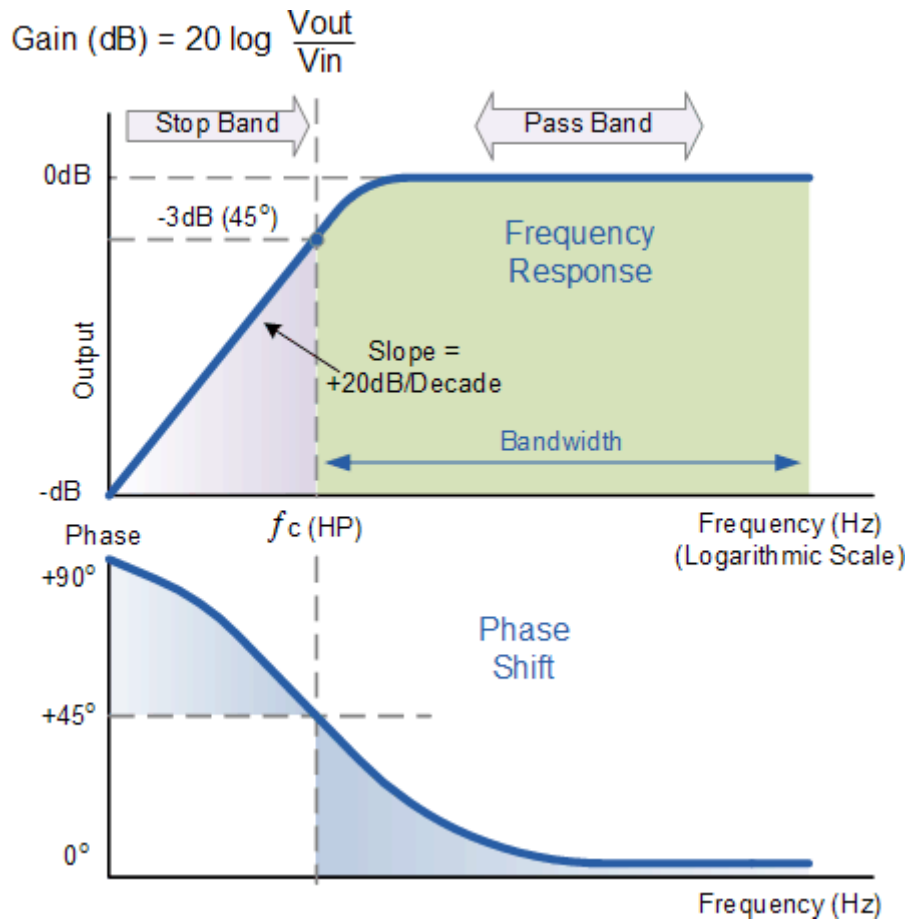
## Frequency Response of a 1st Order High Pass Filter



The **Bode Plot** or Frequency Response Curve above for a passive high pass filter is the exact opposite to that of a low pass filter. Here the signal is attenuated or damped at low frequencies with the output increasing at +20dB/Decade (6dB/Octave) until the frequency reaches the cut-off point ( $f_c$ ) where again  $R = X_c$ . It has a response curve that extends down from infinity to the cut-off frequency, where the output voltage amplitude is  $1/\sqrt{2} = 70.7\%$  of the input signal value or -3dB ( $20 \log (V_{out}/V_{in})$ ) of the input value.

Also we can see that the phase angle ( $\Phi$ ) of the output signal **LEADS** that of the input and is equal to **+45°** at frequency  $f_c$ . The frequency response curve for this filter implies that the filter can pass all signals out to infinity. However in practice, the filter response does not extend to infinity but is limited by the electrical characteristics of the components used.

 The cut-off frequency point for a first order high pass filter can be found using the same equation as that of the low pass filter, but the equation for the phase shift is modified slightly to account for the positive phase angle as shown below.



### Cut-off Frequency and Phase Shift

$$f_c = \frac{1}{2\pi RC}$$

$$\text{Phase Shift } \phi = \arctan \frac{1}{2\pi fRC}$$

The circuit gain,  $A_v$  which is given as  $V_{out}/V_{in}$  (magnitude) and is calculated as:

$$A_v = \frac{V_{OUT}}{V_{IN}} = \frac{R}{\sqrt{R^2 + X_c^2}} = \frac{R}{Z}$$

at low  $f$ :  $X_c \rightarrow \infty$ ,  $V_{out} = 0$   
at high  $f$ :  $X_c \rightarrow 0$ ,  $V_{out} = V_{in}$

### PROCEDURE

1. Start-Electronicworkbench-Multisim14.1.
2. Select the components from place-components library according to the following circuit.
3. Connect the oscilloscope [simulate-instrument-oscilloscope].
4. Simulate-Run.
5. Double click on the Bode plotter.

### OBSERVATION

In the above experiment we observe that the theoretical and practical characteristics curve are different.

### CONCLUSION

From the above experiment we observe that the characteristics of high pass filter.

