


SUB - Analog Electronics & OPAMP

Faculty Name - Ipsita Mohanty

Transistors

- * Transistor is a electronics device which are used for amplification of voltage as well as current.
- * Amplification in transistor is achieved by passing input current signal from a region of low resistance to a region of high resistance. So this device is known as Transistor (Transfer-resistor)

Types of transistor

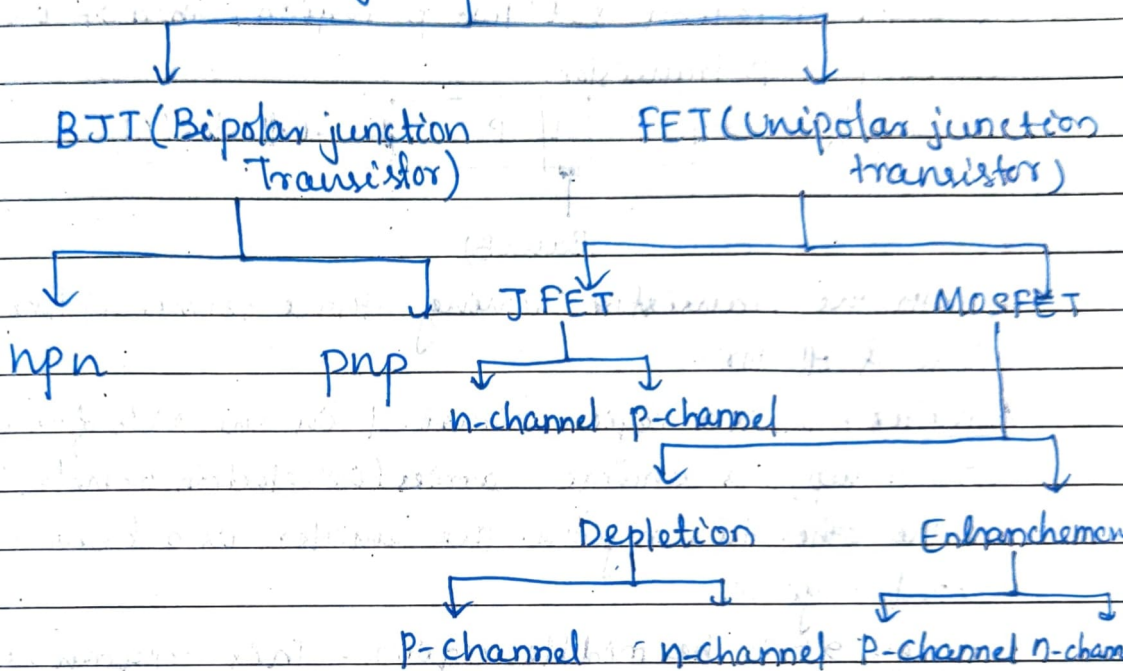


BJT (Bipolar Junction Transistor) :-


- * Basically BJT is called a transistor. It is a three terminal, 3 layer and 2 junction device having the terminal Base, Emitter & Collector.
- * It is operated in three configurations common base, Common Emitter & Common Collector.
- * BJT is called Bipolar Junction transistor because current conduction is due to both type of charge carries i.e. electrons and holes.
- * BJT is also called current controlled device because the output current is controlled by input current.

Construction:-

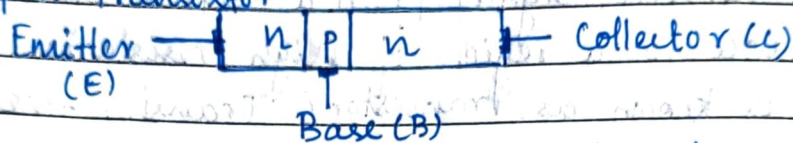* n-p-n:- when a transistor is formed by sandwiching a single p-region betⁿ two n-region, then it is n-p-n transistor



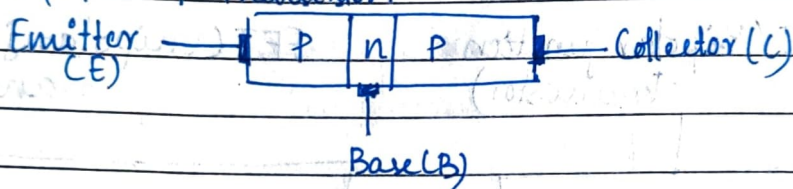* P-n-p:- when a transistor is formed by sandwiching a single n-region betⁿ two p-region, then it is called P-n-P transistor.



* Both the transistor having three terminal Emitter, Base & collector.


* Emitter: It is a region situated in one side of transistor which supplies charge carriers (i.e. electron or holes) to the other two regions. The emitter is a heavily doped region.

* Base: It is the middle region. This region is thin & lightly doped.

* Collector: It is a region situated in the other side of transistor which collects charge carriers (i.e. electrons or holes). The collector of a transistor is always larger than the emitter and base of the transistor & doping level of collector is greater than base but lesser than emitter.

* Junction of transistor: Basically a transistor has two p-n junction. One junction is betⁿ Emitter & Base and another junction is between Base & collector. Junction betⁿ Emitter & Base are called Emitter Base junction & junction betⁿ collector & Base are called collector-Base Junction.

Symbol :-

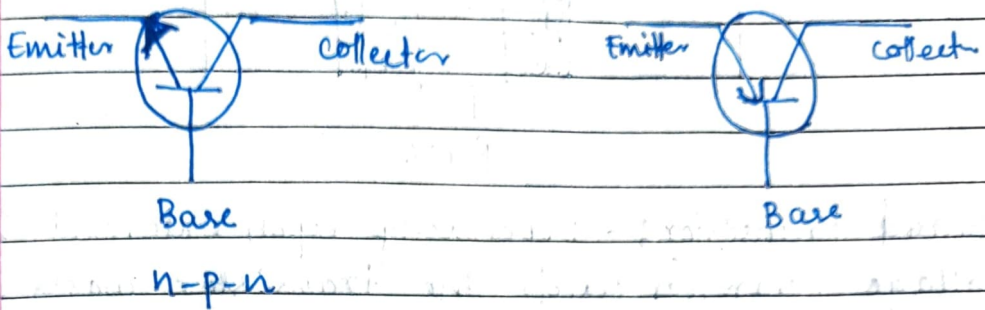

* The arrow mark indicates direction of conventional current.


Transistor Operation :-

* The emitter-base junction of a transistor is forward biased where as collector-base junction is reverse biased.

* ~~It~~

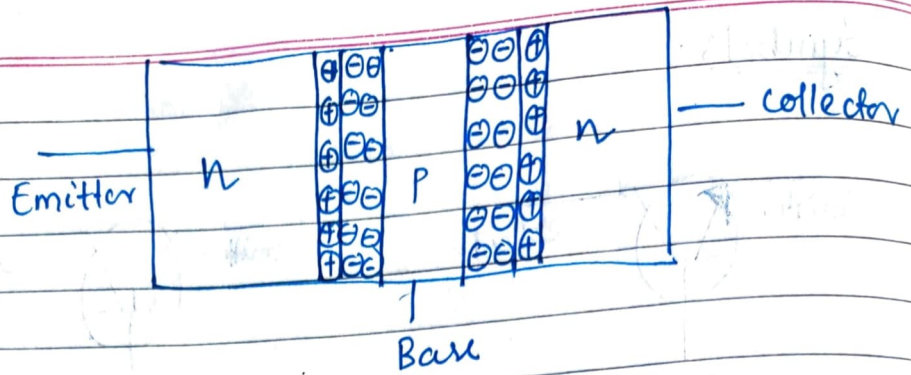(c) unbiased transistor :-


- * It means a transistor with no external voltage is applied. So there is no current conduction in this transistor.
- * Transistor is like two P-n junction diode connected back to back there is a depletion region at both the junction.
- * During diffusion process, depletion region penetrates more deeply into light doped side.
- * Depletion region at emitter junction penetrates less in heavily doped emitter and extends more in base region.
- * Similarly depletion region at collector junction penetrates less in heavily doped collector and extends more in base region.
- * Barrier potential also exists in transistor.
- * The ~~po~~




Biased transistor:- Depending upon external bias voltage polarities used, the transistor works in one of the three regions - active region, cutoff region and saturation region.

Mode of operation:-


Region	Emitter-Base junction	collector-base junction	Function
Active	Forward biased	Reverse biased	Amplifier
Cut off	Reverse biased	Reverse biased	OFF Switch
Saturation	Forward biased	Forward biased	ON Switch

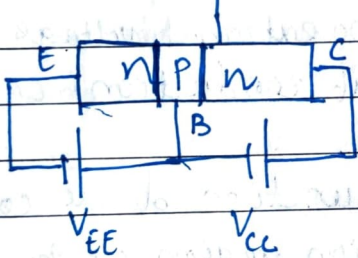

Active region

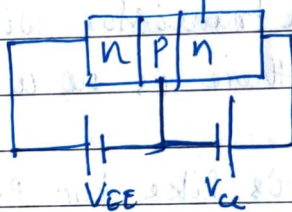

Cutoff

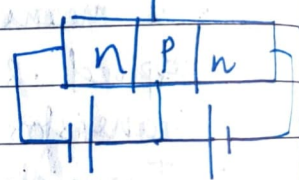

Saturation

* Normally the transistor operates in active region. Due to supply voltage V_{EE} & V_{CC} make the transistor in active region.

operation of n-p-n transistor:-

* The base to emitter junction is forward bias by a dc source V_{EE} . So depletion width at this junction is reduced. The collector to base junction is reverse biased by V_{CC} so depletion

width at this junction is increased.

* The forward biased Emitter - Base (EB) junction causes electrons in the emitter to flow towards the base. This produces the emitter current I_E .

* At the free few electrons recombine with holes in p-region [base] due to lightly doping. Thus such recombination produce the base current I_B . The remaining large no of electrons crosses the base region and moves towards the collector region to Positive terminal of the external source. This produce the collector current I_C .

* Due to this electron flow constitute the current across the transistor.


* The current relation of the transistor is given by $I_E = I_B + I_C$

* Since it is a bipolar device so current is flows due to both minority & majority carriers.


So total The minority component is called the leakage current when input ckt is open and given by symbol I_{CO} .

So total collector current
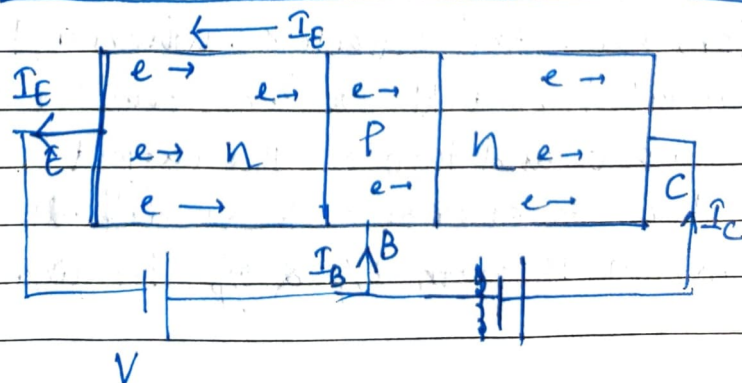
$$I_C = I_{C \text{ majority}} + I_{C \text{ minority}}$$




operation of pnp transistor :-

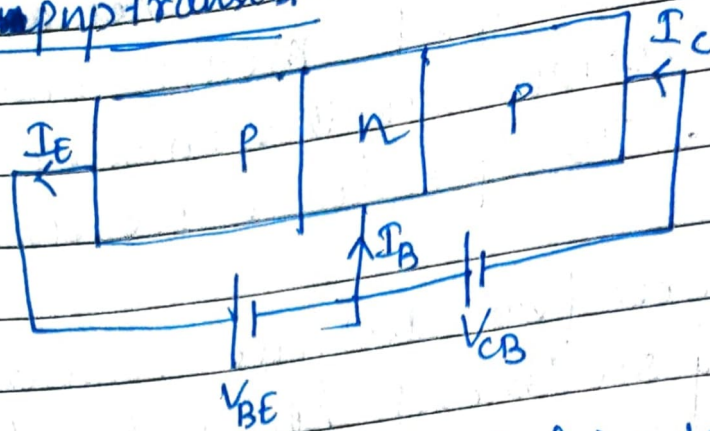

- * The PNP transistor with forward bias to emitter base junction and reverse bias to collector base junction.
- * The forward bias causes the holes in the p-type emitter to flow towards the base. This constitutes the emitter current I_E .
- * As the holes cross into n-type base, they tend to combine with the electron but due to the base is lightly doped ~~so~~ only 5% holes are recombining to form base current. The remaining (more than) cross the collector region constitute the collector current (I_C).
- * Therefore the current conduction of pnp is due to the holes.
- * The input junction (i.e. emitter-base junction) has low resistance due to forward bias and the output ckt has high resistance due to reverse bias.

Current Components in the transistor

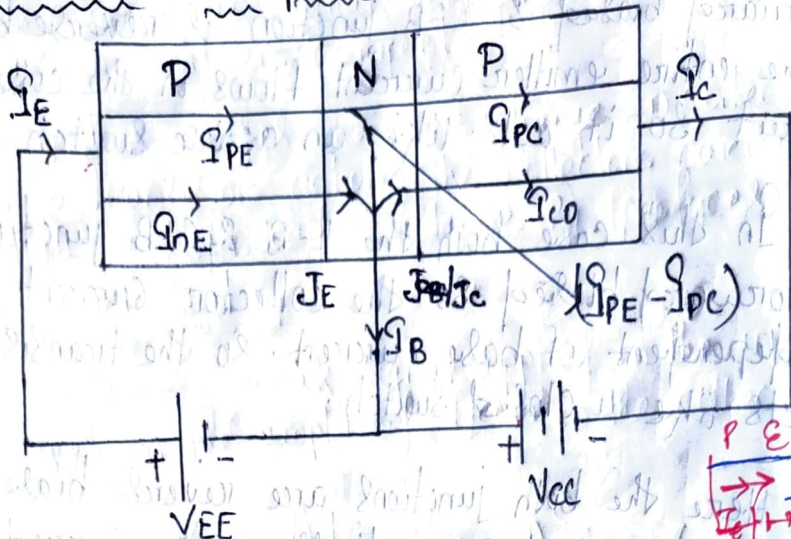

→ Here the hole current I_{PE} constituted by holes. Electron current I_{NE} constituted by electrons.

∴ Total emitter current $I_E = I_{PE} + I_{NE}$

→ we know the doping of emitter region is made much heavier than base and hence the electron current component I_{NE} is negligible small in comparison with hole current I_{PE} .

→ A few ~~electron~~ holes crossing the junction J_E combine with the electrons in N-type base and rest of them cross the collector junction J_C .

→ This reduces the no. of holes which ultimately reach the collector. To reduce the no. of holes so lost through recombination with electrons in N-region, the width of the base region is kept extremely small.

→ Let, I_{PC} = hole current in junction J_C
 $I_{PE} - I_{PC}$ = difference combination current I_B

→ In fact, electrons enter the base region through the base lead to replenish those electrons which have been lost by recombination with the holes injected into the base across J_E .

→ The holes on reaching the collector junction cross this junction readily and enter the P-region of the collector.

→ If the emitter is open circuit then, $I_E = 0$ i.e. I_{pc} would be zero.

→ Under this condition the base and collector together act as a reversed diode & the collector current I_c equals the reverse saturation current I_{co} .

→ I_{nco} caused by electrons moving across J_c from P-region to N-region.

→ I_{pco} caused by holes moving across J_c from N-region to P-region.

$$\Rightarrow I_{co} = I_{nco} + I_{pco} \quad \text{--- (ii)}$$

$$\Rightarrow I_c = I_{pc} + I_{co} \quad \text{--- (iii)}$$

$$\Rightarrow \boxed{I_E = I_B + I_c} \quad \text{--- (iv)}$$


Transistor Circuit Configuration & its characteristics

- i Common - Base Config.
- ii Common - emitter Config.
- iii Common - collector Config.

Common - Base Configuration :-

→ In this circuit arrangement, input is applied between the emitter base junction & output is taken from the collector-base.

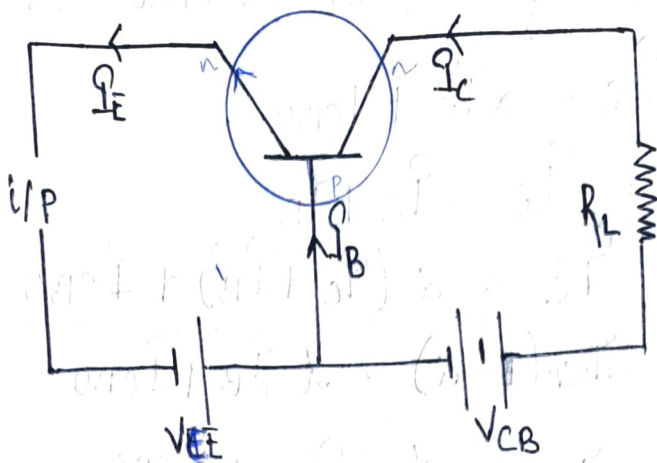→ Here base of the transistor is common to both the input and output of circuit so it is known as common - base configuration.



Current Amplification Factor :-

It is the ratio of change in collector current to the change in emitter current at constant collector base voltage. V_{CB} is known as current amplification factor.

Current Amplification factor (α) → It is the of output current to input current.

$$\text{Input Current} = I_E$$

$$\text{Output Current} = I_C$$

$$\text{So, } \alpha = \frac{\Delta I_C}{\Delta I_E} \text{ at constant } V_{CB}$$

→ Practical value of α in commercial transistor range from 0.9 to 0.99.


Expression for collector current :-

∴ The total collector current $I_C = \alpha I_E + I_{\text{Leakage}}$

→ Here the leakage current is due to movement of minority carriers across base-collector junction, due to reverse biased.

→ It is generally smaller than αI_E .

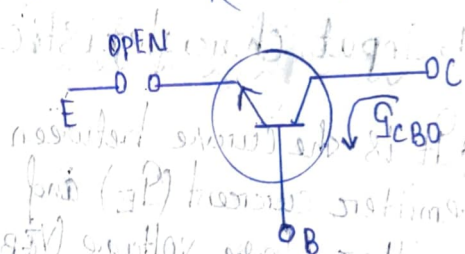→ If the $I_E = 0$, a small leakage current still flow in the collector circuit.



→ So the leakage current is known as I_{CBO} .

$$\therefore I_C = \alpha I_E + I_{CBO}$$

Now, $I_E = I_C + I_B$

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$


$$I_C (1 - \alpha) = \alpha I_B + I_{CBO}$$

$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{I_{CBO}}{1 - \alpha}$$

Characteristics of Common-Base Connection:

→ It is the complete electrical behaviour of transistor current and voltage in graphical curve is known as characteristics of transistor.

1. Input characteristic:

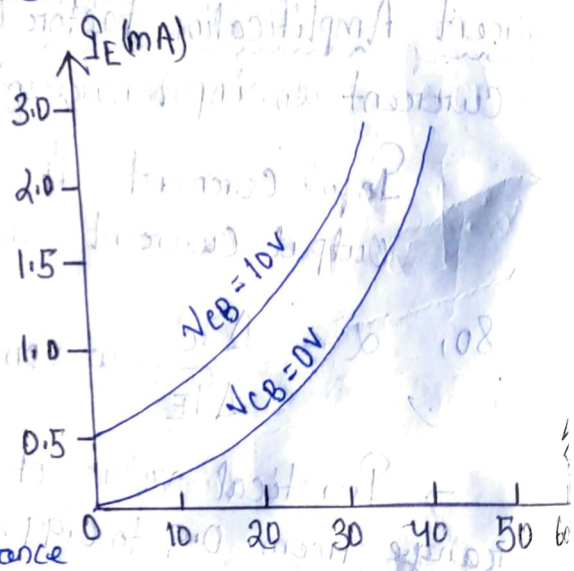


→ It is the curve between emitter current (I_E) and emitter-base voltage (V_{EB}).

→ The emitter current I_E increases rapidly with small increase in emitter-base voltage V_{EB} . i.e. input resistance is very small.

→ Input Resistance → It is the ratio of change in emitter base voltage (ΔV_{EB}) to the change in emitter current at constant collector-base voltage (V_{CB}).

$$\therefore r_i = \frac{\Delta V_{BE}}{\Delta I_E} \text{ at constant } V_{CB}$$

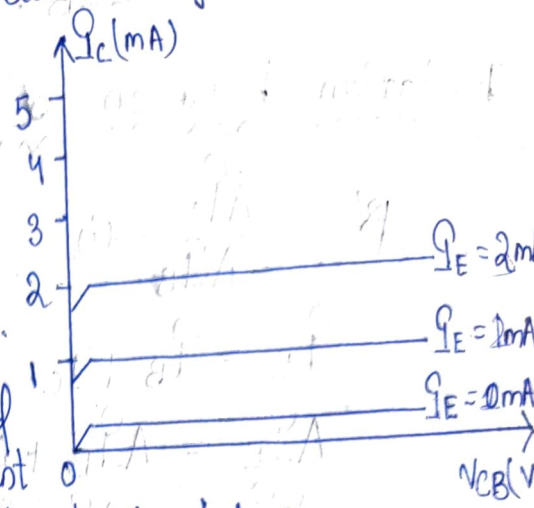2. Output Characteristics :- It is the curve betⁿ collector current (I_C) and collector-base voltage (V_{CB}) at constant emitter current (I_E).



→ The collector current I_C varies with V_{CB} only at very low voltage ($< 1V$). The transistor is never operated in this region.

→ when the value of V_{CB} raised above 1-2 V, the collector current becomes constant as indicated by horizontal curve.

→ It means that now I_C is independent of V_{CB} and depend upon I_E only.


Output Resistance :- It is the ratio of change in collector-base voltage to the collector current.

$$\therefore r_o = \frac{\Delta V_{CB}}{\Delta I_C} \text{ at constant } I_E$$

Common Emitter Connection :-

→ Here the input is applied between base emitter and output is taken from collector emitter junction.

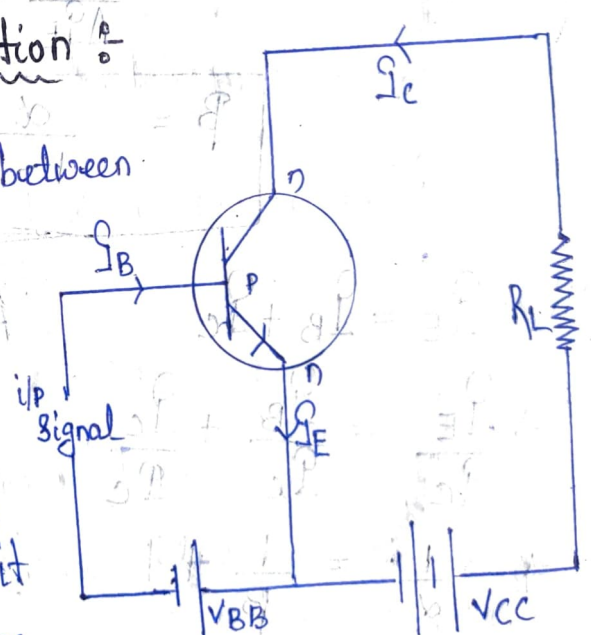→ Here emitter of the transistor is common to both input and output so hence it is known as common emitter connection.



Base Current Amplification factor (β) → It is the ratio of change in collector current to base current (I_B).

$$\beta = \frac{\Delta I_c}{\Delta I_B}$$

Relation between α and β :

$$\beta = \frac{\Delta I_c}{\Delta I_B} \quad \text{--- (i)}$$

$$\alpha = \frac{\Delta I_c}{\Delta I_E} \quad \text{--- (ii)}$$

$$I_E = I_B + I_c$$

$$\Delta I_E = \Delta I_B + \Delta I_c$$

$$\Delta I_B = \Delta I_E - \Delta I_c$$

Substituting the value of ΔI_B in eq (i)

$$\beta = \frac{\Delta I_c}{\Delta I_E - \Delta I_c}$$

Dividing ΔI_E in both numerator and denominator

$$\beta = \frac{\Delta I_c / \Delta I_E}{\frac{\Delta I_E - \Delta I_c}{\Delta I_E}} = \frac{\alpha}{1 - \alpha} \quad \left[\because \alpha = \frac{\Delta I_c}{\Delta I_E} \right]$$

$$\boxed{\beta = \frac{\alpha}{1 - \alpha}}$$

OR $I_E = I_B + I_c$

$$\Rightarrow \frac{I_E}{I_c} = \frac{I_B}{I_c} + \frac{I_c}{I_c}$$

$$\Rightarrow \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\Rightarrow \alpha = \frac{\beta}{1 + \beta}$$

Again, $\frac{1}{\beta} = \frac{1}{\alpha} - 1$

$$\Rightarrow \frac{1}{\beta} = \frac{1 - \alpha}{\alpha}$$

$$\Rightarrow \beta = \frac{\alpha}{1 - \alpha}$$

Expression for collector current

we know,

$$I_E = I_B + I_C \quad \text{--- (i)}$$

$$I_C = \alpha I_E + I_{CBO} \quad \text{--- (ii)}$$

$$I_C = \alpha I_E + I_{CBO} = \alpha (I_B + I_C) + I_{CBO}$$

$$I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO} \quad \text{--- (iii)}$$

If the value of $I_B = 0$, then

$$I_{CEO} = \frac{1}{1-\alpha} I_{CBO}$$

Substituting the value of $I_{CEO} = \frac{1}{1-\alpha} I_{CBO}$ in eqn (iii)

$$I_C = \frac{\alpha}{1-\alpha} I_B + I_{CEO}$$

OR

$$I_C = \beta I_B + I_{CEO} \quad \left(\because \beta = \frac{\alpha}{1-\alpha} \right)$$

Characteristics of Common Emitter Connection


1. Input characteristic - It is the curve between base current I_B and base emitter voltage V_{BE} at constant collector emitter voltage V_{CE}

→ Input resistance of a CE circuit is higher than of CB circuit.


Input Resistance

It is the ratio of change in base-emitter voltage to base current, at constant V_{CE} .
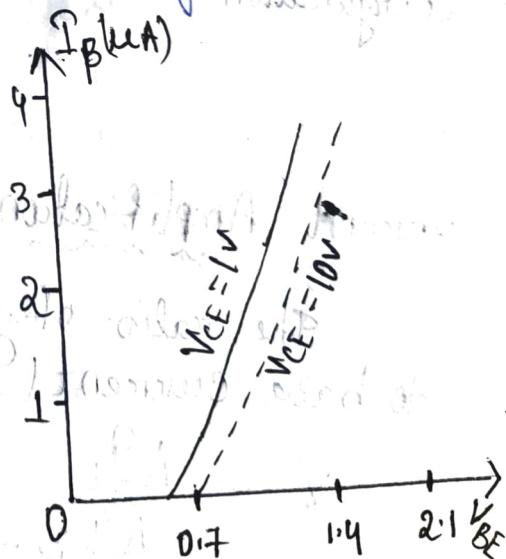
$$\therefore r_i = \frac{\Delta V_{BE}}{\Delta I_B} \quad \text{at constant } V_{CE}$$



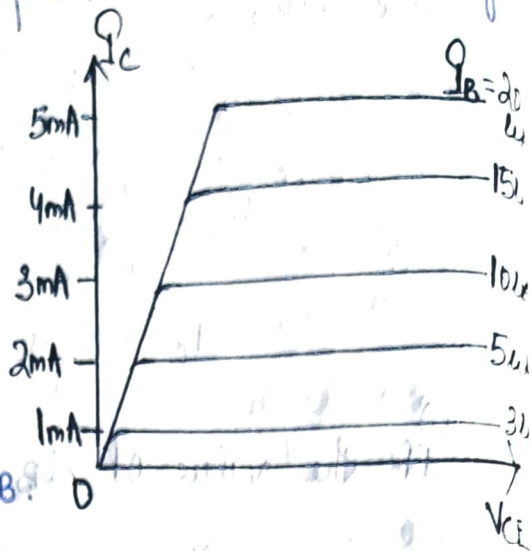Output characteristic → It is the curve between collector current I_c and collector emitter voltage V_{CE} at constant I_B .



Output Resistance :-


→ It is the ratio of change in collector-emitter voltage to collector current.

$$\therefore r_{co} = \frac{\Delta V_{CE}}{\Delta I_c} \text{ at constant } I_B$$

Common Collector Connection :-

→ Here input is applied in both base and collector and o/p is taken from the emitter collector.

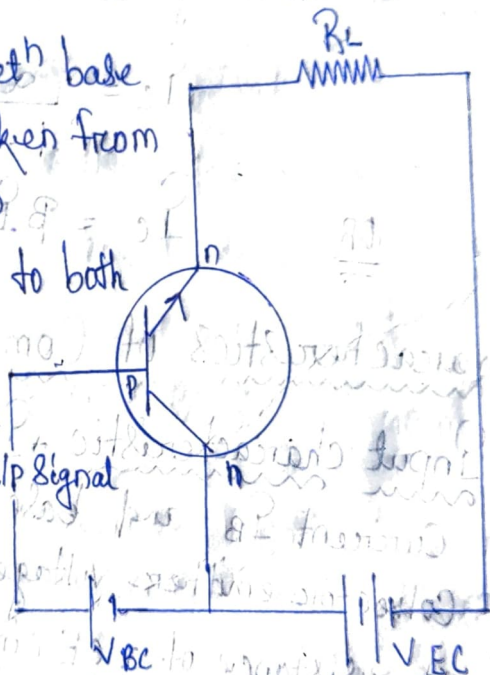→ Here collector is common to both i/p and o/p of circuit so its name is common collector Configuration.



Current Amplification Factor (γ) :-

The ratio of change in emitter current (I_E) to base current (I_B).

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$\gamma = \frac{\Delta I_c + \Delta I_B}{\Delta I_B}$$

$$= \frac{\Delta I_c / \Delta I_B + \Delta I_B / \Delta I_B}{\Delta I_B / \Delta I_B}$$

$$\Rightarrow \boxed{\gamma = \beta + 1}$$

$$\text{So, } \gamma = \beta + 1$$

$$= \frac{\alpha}{1-\alpha} + 1$$

$$= \frac{\alpha + 1 - \alpha}{1-\alpha} \Rightarrow \gamma = \frac{1}{1-\alpha}$$

Expression for Collector Current:

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_B + I_C = I_B + (\alpha I_E + I_{CBO})$$

$$\Rightarrow I_E (1-\alpha) = I_B + I_{CBO}$$

$$\Rightarrow I_E = \frac{I_B}{1-\alpha} + \frac{I_{CBO}}{1-\alpha}$$

$$\Rightarrow I_E = \frac{1}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

$$I_C \approx I_E = \gamma I_B + \gamma I_{CBO}$$

$$= (\beta + 1) I_B + (\beta + 1) I_{CBO}$$

Application: - This circuit has very high i/p resistance and very low o/p resistance. Due to this reason it is used for impedance matching.

